

ASIC LIBRARY DESIGN

3

Key concepts: Tau, logical effort, and the prediction of delay • Sizes of cells, and their drive strengths • Cell importance • The difference between gate-array macros, standard cells, and datapath cells

ASIC design uses predefined and precharacterized cells from a library—so we need to design or buy a cell library. A knowledge of ASIC library design is not necessary but makes it easier to use library cells effectively.


3.1 Transistors as Resistors

$$0.35V_{DD} = V_{DD} \exp\left(\frac{-t_{PDf}}{R_{pd}(C_{out} + C_p)}\right)$$

An output trip point of 0.35 is convenient because $\ln(1/0.35) = 1.04$ and thus




$$t_{PDf} = R_{pd}(C_{out} + C_p) \ln(1/0.35) = R_{pd}(C_{out} + C_p)$$

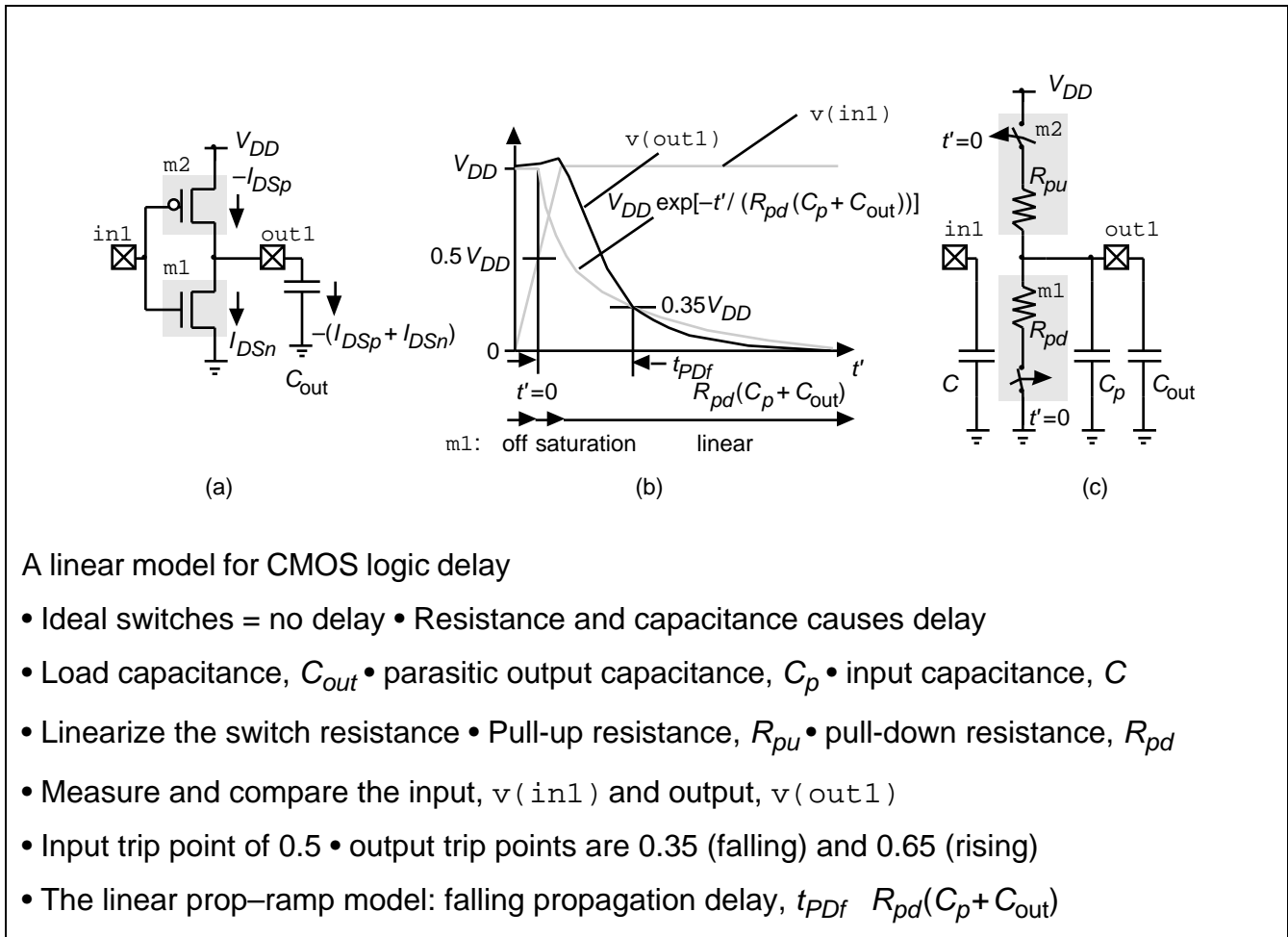For output trip points of 0.1/0.9 we multiply by $-\ln(0.1) = 2.3$, because $\exp(-2.3) = 0.100$



A linear model for CMOS logic delay


- Ideal switches = no delay • Resistance and capacitance causes delay
- Load capacitance, C_{out} • parasitic output capacitance, C_p • input capacitance, C
- Linearize the switch resistance • Pull-up resistance, R_{pu} • pull-down resistance, R_{pd}
- Measure and compare the input, $v(in1)$ and output, $v(out1)$
- Input trip point of 0.5 • output trip points are 0.35 (falling) and 0.65 (rising)
- The linear prop-ramp model: falling propagation delay, $t_{PDf} R_{pd}(C_p + C_{out})$

   

CMOS inverter characteristics

- Equilibrium switching
- Non-equilibrium switching
- Nonlinear switching resistance
- Switching current

3.2 Transistor Parasitic Capacitance

 

Transistor parasitic capacitance

- Constant overlap capacitances C_{GSOV} , C_{GDOV} , and C_{GBOV}
- Variable capacitances C_{GS} , C_{GB} , and C_{GD} depend on the operating region
- C_{BS} and C_{BD} are the sum of the area (C_{BSJ} , C_{BDJ}), sidewall (C_{BSSW} , C_{BDSW}), and channel edge ($C_{BSJGATE}$, $C_{BDJGATE}$) capacitances
- L_D is the lateral diffusion • T_{FOX} is the field-oxide thickness

NAME	m1	m2
MODEL	CMOSN	CMOSP
ID	7.49E-11	-7.49E-11
VGS	0.00E+00	-3.00E+00
VDS	3.00E+00	-4.40E-08
VBS	0.00E+00	0.00E+00
VTH	4.14E-01	-8.96E-01
VDSAT	3.51E-02	-1.78E+00
GM	1.75E-09	2.52E-11
GDS	1.24E-10	1.72E-03
GMB	6.02E-10	7.02E-12
CBD	2.06E-15	1.71E-14
CBS	4.45E-15	1.71E-14
CGSOV	1.80E-15	2.88E-15
CGDOV	1.80E-15	2.88E-15
CGBOV	2.00E-16	2.01E-16
CGS	0.00E+00	1.10E-14
CGD	0.00E+00	1.10E-14
CGB	3.88E-15	0.00E+00

- ID (I_{DS}), VGS, VDS, VBS, VTH (V_t), and VDSAT ($V_{DS(sat)}$) are DC parameters
- GM, GDS, and GMB are small-signal conductances (corresponding to I_{DS}/V_{GS} , I_{DS}/V_{DS} , and I_{DS}/V_{BS} , respectively)

Calculations of parasitic capacitances for an n-channel MOS transistor.		
PSpice	Equation	Values ¹ for $V_{GS}=0V, V_{DS}=3V, V_{SB}=0V$
CBD	$C_{BD} = C_{BDJ} + C_{BDSW}$ $C_{BDJ} + A_D C_J (1 + V_{DB}/V_B)^{-m_J} \quad (V_B = V_{PB})$ $C_{BDSW} = P_D C_{JSW} (1 + V_{DB}/V_B)^{-m_{JSW}}$ (P_D may or may not include channel edge)	$C_{BD} = 1.855 \times 10^{-13} + 2.04 \times 10^{-16} = 2.06 \times 10^{-13} \text{ F}$ $C_{BDJ} = (4.032 \times 10^{-15})(1 + (3/1))^{-0.56} = 1.86 \times 10^{-15} \text{ F}$ $C_{BDSW} = (4.2 \times 10^{-16})(1 + (3/1))^{-0.5} = 2.04 \times 10^{-16} \text{ F}$
CBS	$C_{BS} = C_{BSJ} + C_{BSSW}$ $C_{BSJ} + A_S C_J (1 + V_{SB}/V_B)^{-m_J}$ $C_{BSSW} = P_S C_{JSW} (1 + V_{SB}/V_B)^{-m_{JSW}}$	$C_{BS} = 4.032 \times 10^{-15} + 4.2 \times 10^{-16} = 4.45 \times 10^{-15} \text{ F}$ $A_S C_J = (7.2 \times 10^{-15})(5.6 \times 10^{-4}) = 4.03 \times 10^{-15} \text{ F}$ $P_S C_{JSW} = (8.4 \times 10^{-6})(5 \times 10^{-11}) = 4.2 \times 10^{-16} \text{ F}$
CGSOV	$C_{GSOV} = W_{EFF} C_{GSO} ; W_{EFF} = W - 2W_D$	$C_{GSOV} = (6 \times 10^{-6})(3 \times 10^{-10}) = 1.8 \times 10^{-16} \text{ F}$
CGDOV	$C_{GDOV} = W_{EFF} C_{GSO}$	$C_{GDOV} = (6 \times 10^{-6})(3 \times 10^{-10}) = 1.8 \times 10^{-15} \text{ F}$
CGBOV	$C_{GBOV} = L_{EFF} C_{GBO} ; L_{EFF} = L - 2L_D$	$C_{GDOV} = (0.5 \times 10^{-6})(4 \times 10^{-10}) = 2 \times 10^{-16} \text{ F}$
CGS	$C_{GS}/C_O = 0$ (off), 0.5 (lin.), 0.66 (sat.) C_O (oxide capacitance) = $W_{EF} L_{EFF} \epsilon_{ox} / T_{ox}$	$C_O = (6 \times 10^{-6})(0.5 \times 10^{-6})(0.00345) = 1.03 \times 10^{-14} \text{ F}$ $C_{GS} = 0.0 \text{ F}$
CGD	$C_{GD}/C_O = 0$ (off), 0.5 (lin.), 0 (sat.)	$C_{GD} = 0.0 \text{ F}$
CGB	$C_{GB} = 0$ (on), = C_O in series with C_{GS} (off)	$C_{GB} = 3.88 \times 10^{-15} \text{ F}$, C_S =depletion capacitance
¹ Input	.MODEL CMOSN NMOS LEVEL=3 PHI=0.7 TOX=10E-09 XJ=0.2U TPG=1 VTO=0.65 DELTA=0.7 + LD=5E-08 KP=2E-04 UO=550 THETA=0.27 RSH=2 GAMMA=0.6 NSUB=1.4E+17 NFS=6E+11 + VMAX=2E+05 ETA=3.7E-02 KAPPA=2.9E-02 CGDO=3.0E-10 CGSO=3.0E-10 CGBO=4.0E-10 + CJ=5.6E-04 MJ=0.56 CJSW=5E-11 MJSW=0.52 PB=1 m1 out1 in1 0 0 cmosn W=6U L=0.6U AS=7.2P AD=7.2P PS=8.4U PD=8.4U	

3.2.1 Junction Capacitance


- Junction capacitances, C_{BD} and C_{BS} , consist of two parts: junction area and sidewall
- Both C_{BD} and C_{BS} have different physical characteristics with parameters: C_J and M_J for the junction, C_{JSW} and M_{JSW} for the sidewall, and P_B is common
- C_{BD} and C_{BS} depend on the voltage across the junction (V_{DB} and V_{SB})
- The sidewalls facing the channel ($C_{BSJGATE}$ and $C_{BDJGATE}$) are different from the sidewalls that face the field
- It is a mistake to exclude the gate edge assuming it is in the rest of the model—it is not
- In HSPICE there is a separate mechanism to account for the channel edge capacitance (using parameters ACM and $CJGATE$)

3.2.2 Overlap Capacitance

- The overlap capacitance calculations for C_{GSOV} and C_{GDOV} account for lateral diffusion
- SPICE parameter $LD=5E-08$ or $L_D=0.05\mu m$
- Not all SPICE versions use the equivalent parameter for width reduction, WD , in calculating C_{GDOV}
- Not all SPICE versions subtract W_D to form W_{EFF}

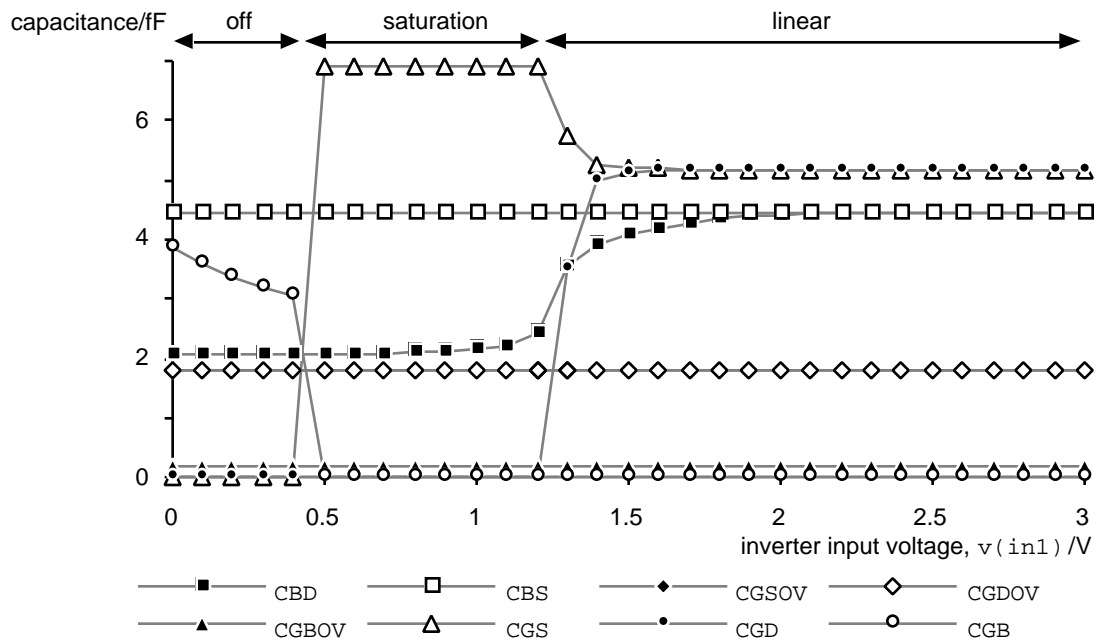3.2.3 Gate Capacitance


- The gate capacitance depends on the operating region
- The gate–source capacitance C_{GS} varies from zero (off) to $0.5C_O$ in the linear region to $(2/3)C_O$ in the saturation region
- The gate–drain capacitance C_{GD} varies from zero (off) to $0.5C_O$ (linear region) and back to zero (saturation region)
- The gate–bulk capacitance C_{GB} is two capacitors in series: the fixed gate-oxide capacitance, C_O , and the variable depletion capacitance, C_S
- As the transistor turns on the channel shields the bulk from the gate—and C_{GB} falls to zero
- Even with $V_{GS}=0V$, the depletion width under the gate is finite and thus C_{GB} is less than C_O




The variation of n-channel transistor parasitic capacitance

- PSpice v5.4 (LEVEL=3)
- Created by varying the input voltage, $v(in1)$, of an inverter
- Data points are joined by straight lines
- Note that $CGSOV=CGDOV$

3.2.4 Input Slew Rate

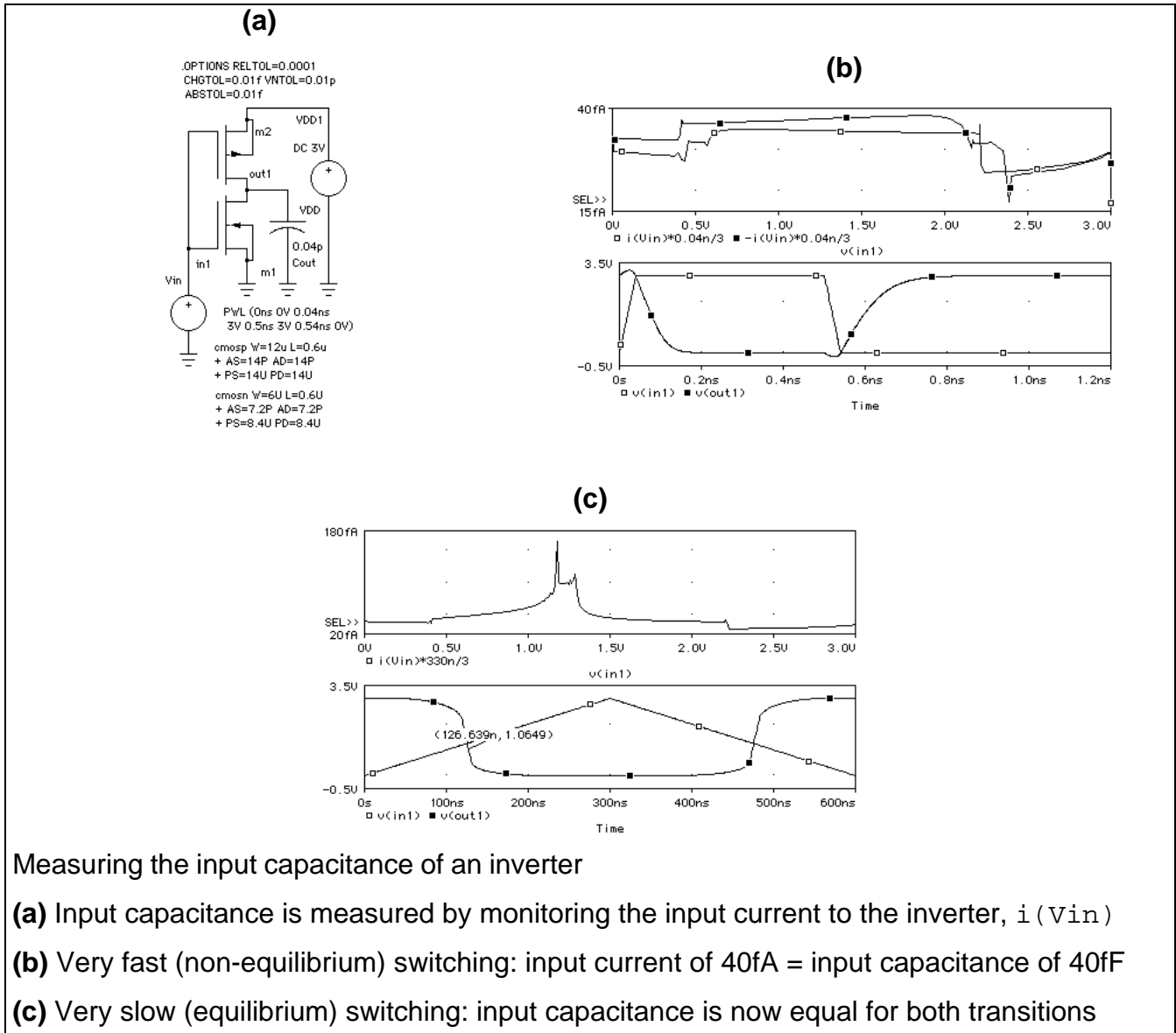

 

Parasitic capacitance measurement

(a) All devices in this circuit include parasitic capacitance

(b) This circuit uses linear capacitors to model the parasitic capacitance of m9 / 10.

- The load formed by the inverter (m5 and m6) is modeled by a 0.0335pF capacitor (c2)
- The parasitic capacitance due to the overlap of the gates of m3 and m4 with their source, drain, and bulk terminals is modeled by a 0.01pF capacitor (c3)
- The effect of the parasitic capacitance at the drain terminals of m3 and m4 is modeled by a 0.025pF capacitor (c4)

(c) Comparison of (a) and (b). The delay (1.22–1.135=0.085ns) is equal to t_{PDf} for the inverter m3 / 4

(d) An exact match would have both waveforms equal at the 0.35 trip point (1.05V).

3.3 Logical Effort

We extend the prop-ramp model with a “catch all” term, t_q , that includes:

- delay due to internal parasitic capacitance
- the time for the input to reach the switching threshold of the cell
- the dependence of the delay on the slew rate of the input waveform

$$t_{PD} = R(C_{out} + C_p) + t_q$$

We can **scale** any logic cell by a scaling factor s : $t_{PD} = (R/s) \cdot (C_{out} + sC_p) + st_q$

$$t_{PD} = RC \frac{C_{out}}{C_{in}} + RC_p + st_q$$

$$\text{Normalizing the delay: } d = \frac{(RC) (C_{out} / C_{in}) + RC_p + st_q}{RC} = f + p + q$$

The time constant $\tau_{inv} = R_{inv} C_{inv}$, is a basic property of any CMOS technology

The delay equation is the sum of three terms, $d = f + p + q$ or
 delay = **effort delay** + **parasitic delay** + **nonideal delay**

The effort delay f is the product of **logical effort**, g , and **electrical effort**, h : $f = gh$

Thus, delay = logical effort \times electrical effort + parasitic delay + nonideal delay

- R and C will change as we scale a logic cell, but the RC product stays the same
- Logical effort is independent of the size of a logic cell
- We can find logical effort by scaling a logic cell to have the same drive as a 1X minimum-size inverter
- Then the logical effort, g , is the ratio of the input capacitance, C_{in} , of the 1X logic cell to C_{inv}

1 Measure the input capacitance of a minimum-size inverter.
 $C_{inv} = 2 + 1 = 3$

2 Make the cell have the same drive strength as a minimum-size inverter.

3 Measure ratio of cell input capacitance to that of a minimum-size inverter.
 $g = C_{in}/C_{inv} = 4/3$

(a) (b) (c)

Logical effort • For a two-input NAND cell, the logical effort, $g=4/3$

(a) Find the input capacitance, C_{inv} , looking into the input of a minimum-size inverter in terms of the gate capacitance of a minimum-size device

(b) Size a logic cell to have the same drive strength as a minimum-size inverter (assuming a logic ratio of 2). The input capacitance looking into one of the logic-cell terminals is then C_{in}

(c) The logical effort of a cell is C_{in}/C_{inv}

The h depends only on the load capacitance C_{out} connected to the output of the logic cell and the input capacitance of the logic cell, C_{in} ; thus

electrical effort $h = C_{out}/C_{in}$

parasitic delay $p = RC_p'$ (the parasitic delay of a minimum-size inverter is: $p_{inv} = C_p'/C_{inv}$)

nonideal delay $q = st_q'$

Cell effort, parasitic delay, and nonideal delay (in units of) for single-stage CMOS cells				
Cell	Cell effort (logic ratio=2)	Cell effort (logic ratio=r)	Parasitic delay/	Nonideal delay/
inverter	1 (by definition)	1 (by definition)	p_{inv} (by definition)	q_{inv} (by definition)
n-input NAND	$(n+2)/3$	$(n+r)/(r+1)$	np_{inv}	nq_{inv}
n-input NOR	$(2n+1)/3$	$(nr+1)/(r+1)$	np_{inv}	nq_{inv}

3.3.1 Predicting Delay

- Example: predict the delay of a three-input NOR logic cell
- 2X drive
- driving a net with a fanout of four
- 0.3pF total load capacitance (input capacitance of cells we are driving plus the interconnect)
- $p=3p_{inv}$ and $q=3q_{inv}$ for this cell
- the input gate capacitance of a 1X drive, three-input NOR logic cell is equal to gC_{inv}
- for a 2X logic cell, $C_{in} = 2gC_{inv}$

$$gh = g \frac{C_{out}}{C_{in}} = \frac{g \cdot (0.3 \text{ pF})}{2gC_{inv}} = \frac{(0.3 \text{ pF})}{(2) \cdot (0.036 \text{ pF})} \quad (\text{Notice } g \text{ cancels out in this equation})$$

The delay of the NOR logic cell, in units of τ , is thus

$$d = gh + p + q = \frac{0.3 \times 10^{-12}}{(2) \cdot (0.036 \times 10^{-12})} + (3) \cdot (1) + (3) \cdot (1.7)$$

$$= 4.1666667 + 3 + 5.1$$

$$= 12.266667 \quad \text{equivalent to an absolute delay, } t_{PD} = 12.3 \times 0.06 \text{ ns} = 0.74 \text{ ns}$$



The delay for a 2X drive, three-input NOR logic cell is $t_{PD} = (0.03 + 0.72C_{out} + 0.60) \text{ ns}$

With $C_{out} = 0.3 \text{ pF}$, $t_{PD} = 0.03 + (0.72) \cdot (0.3) + 0.60 = 0.846 \text{ ns}$ compared to our prediction of 0.74ns

  3.3.2 Logical Area and Logical Efficiency



An OAI221 logic cell

- **Logical-effort vector $g=(7/3, 7/3, 5/3)$**
- **The logical area is 33 logical squares**



An AOI221 logic cell

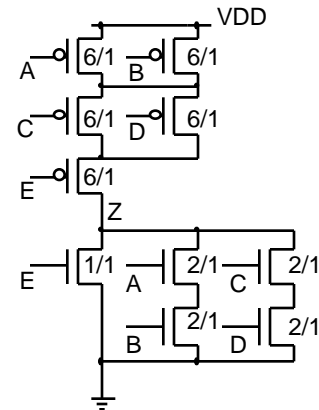 - **$g=(8/3, 8/3, 7/3)$**
- **Logical area is 39 logical squares**
- **Less logically efficient than OAI221**



3.3.3 Logical Paths

$$\text{path delay } D = \sum_i g_i h_i + \sum_i (p_i + q_i)$$

3.3.4 Multistage Cells

(a)

$g_0=1$ $g_2=1.4$
 $p_0=1$ $p_2=2$
 $q_0=1.7$ $q_2=3.4$
 $g_3=1.4$ $p_3=2$ $q_3=3.4$ AOI221
 $g_4=1$ $p_4=1$ $q_4=1.7$
 $g_1=(2, 1.6)$
 $p_1=3$
 $q_1=5.4$

delay d_1
 $h_0=1.4$ $h_2=1.0$
 $h_3=0.7$
 $h_4=C_L$

$$d_1 = (g_0 h_0 + p_0 + q_0) + (g_2 h_2 + p_2 + q_2) + (g_3 h_3 + p_3 + q_3) + (g_4 h_4 + p_4 + q_4)$$

$$= (1 \times 1.4 + 1 + 1.7) + (1.4 \times 1 + 2 + 3.4) + (1.4 \times 0.7 + 2 + 3.4) + (1 \times C_L + 1 + 1.7) = 20 + C_L$$

(b)

$g_0=1$
 $p_0=1$
 $q_0=1.7$
 $g_1=(2.6, 2.6, 2.2)$
 $p_1=5$
 $q_1=8.5$

delay d_1
 C_L

$$d_1 = (1 \times 2.6 + 1 + 1.7) + (1 \times C_L + 5 + 8.5) = 18.8 + C_L$$

(b) is slightly faster than (a)

Logical paths • Comparison of multistage and single-stage implementations

(a) An AOI221 logic cell constructed as a multistage cell, $d_1 = 20 + C_L$

(b) A single-stage AOI221 logic cell, $d_1 = 18.8 + C_L$

3.3.5 Optimum Delay

path logical effort $G = \prod_{i \text{ path}} g_i$

path electrical effort $H = \prod_{i \text{ path}} h_i \frac{C_{out}}{C_{in}}$

C_{out} is the load and C_{in} is the first input capacitance on the path


path effort $F = GH$

optimum effort delay $f_i = g_i h_i = F^{1/N}$

optimum path delay $D^* = NF^{1/N} = N(GH)^{1/N} + P + Q$

$$P + Q = \prod_{i \text{ path}} p_i + h_i$$

3.3.6 Optimum Number of Stages

 


- Chain of N inverters each with equal stage effort, $f = gh$
- Total path delay is $Nf = Ngh = Nh$, since $g = 1$ for an inverter

- To drive a path electrical effort H , $h^N=H$, or $N\ln h=\ln H$
- Delay, $Nh = h\ln H/\ln h$
- Since $\ln H$ is fixed, we can only vary $h/\ln(h)$
- $h/\ln(h)$ is a shallow function with a minimum at $h=e \approx 2.718$
- Total delay is $Ne=e\ln H$

3.4 Library-Cell Design


- A big problem in library design is dealing with design rules
- Sometimes we can **waive** design rules
- **Symbolic layout, sticks** or **logs** can decrease the library design time (9 months for Virtual Silicon—currently the most sophisticated standard-cell library)
- Mapping symbolic layout uses 10–20 percent more area (5–10 percent with compaction)
- Allowing 45° layout decreases silicon area (some companies do not allow 45° layout)

3.5 Library Architecture

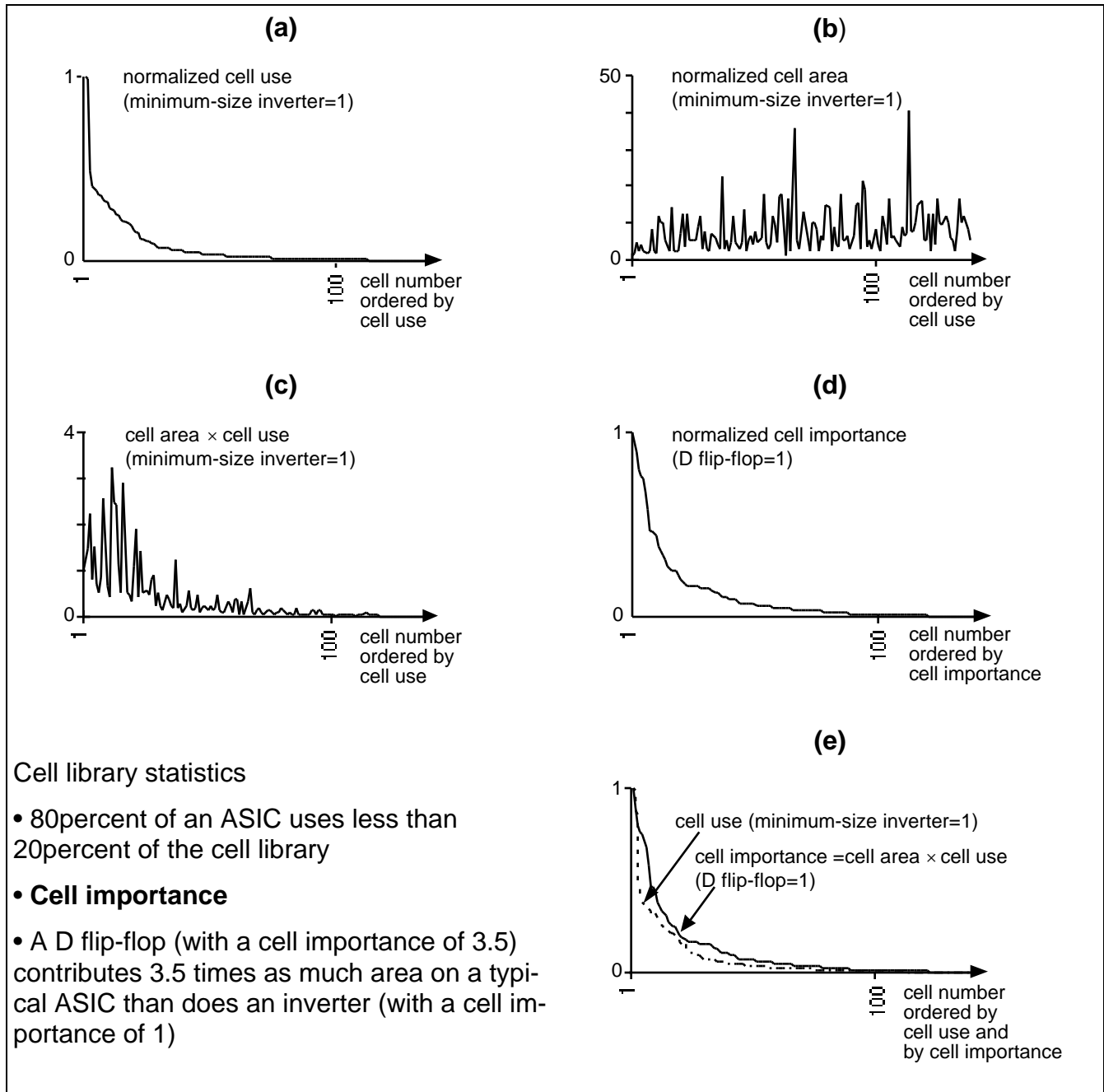

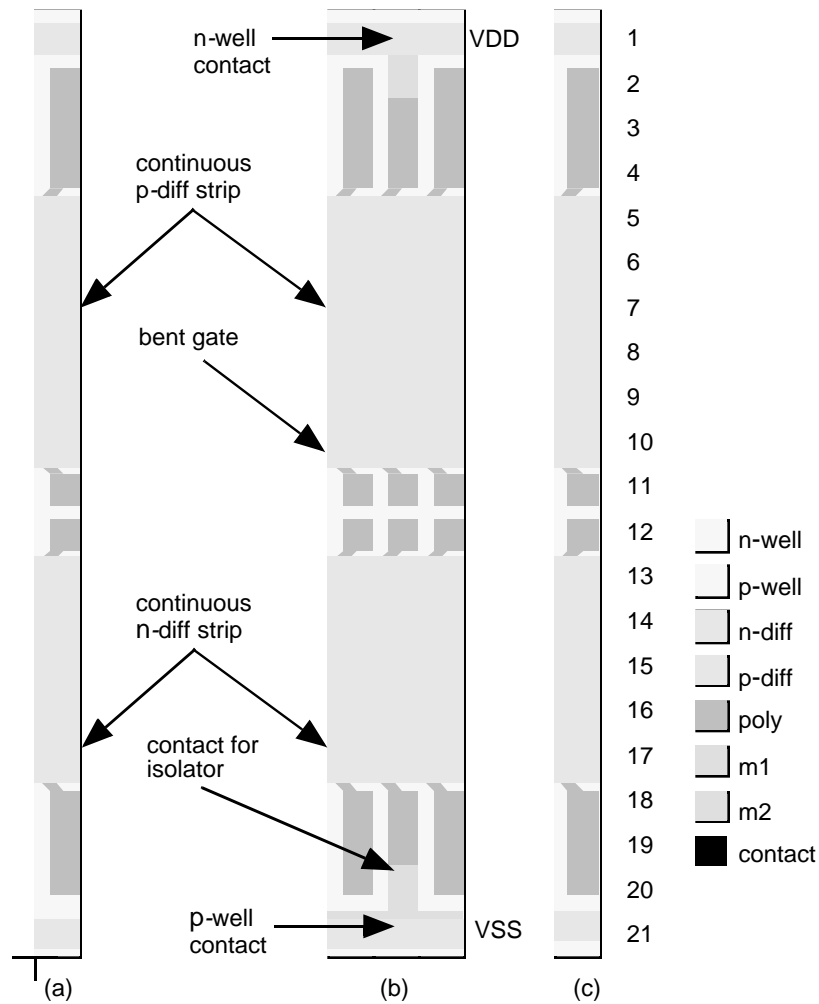3.6 Gate-Array Design

Key words: gate-array base cell (or base cell) • gate-array base (or base) • horizontal tracks • vertical track • gate isolation • isolator transistor • oxide isolation • oxide-isolated gate array





The construction of a gate-isolated gate array

(a) The one-track-wide base cell containing one p-channel and one n-channel transistor

(b) The center base cell is isolating the base cells on either side from each other

 
(c) The base cell is 21 tracks high (high for a modern cell library)



 


An oxide-isolated gate-array base cell

 - 14 tracks high and 4 tracks wide
- VDD (tracks 3 and 4) and GND (tracks 11 and 12) are each 2 tracks wide
- 10 horizontal routing tracks (tracks 1, 2, 5–10, 13, 14)—unusually large number for modern cells
- p-channel and n-channel polysilicon **bent gates** are tied together in the center of the cell
- The well contacts leave room for a **poly cross-under** in each base cell.




Flip-flop macro in a gate-isolated gate-array library

 - Only the first-level metallization and contact pattern, the **personalization**, is shown, but this is enough information to derive the schematic
- This is an older topology for 2LM (cells for 3LM are shorter in height)




The SiARC/Synopsys cell-based array (CBA) basic cell

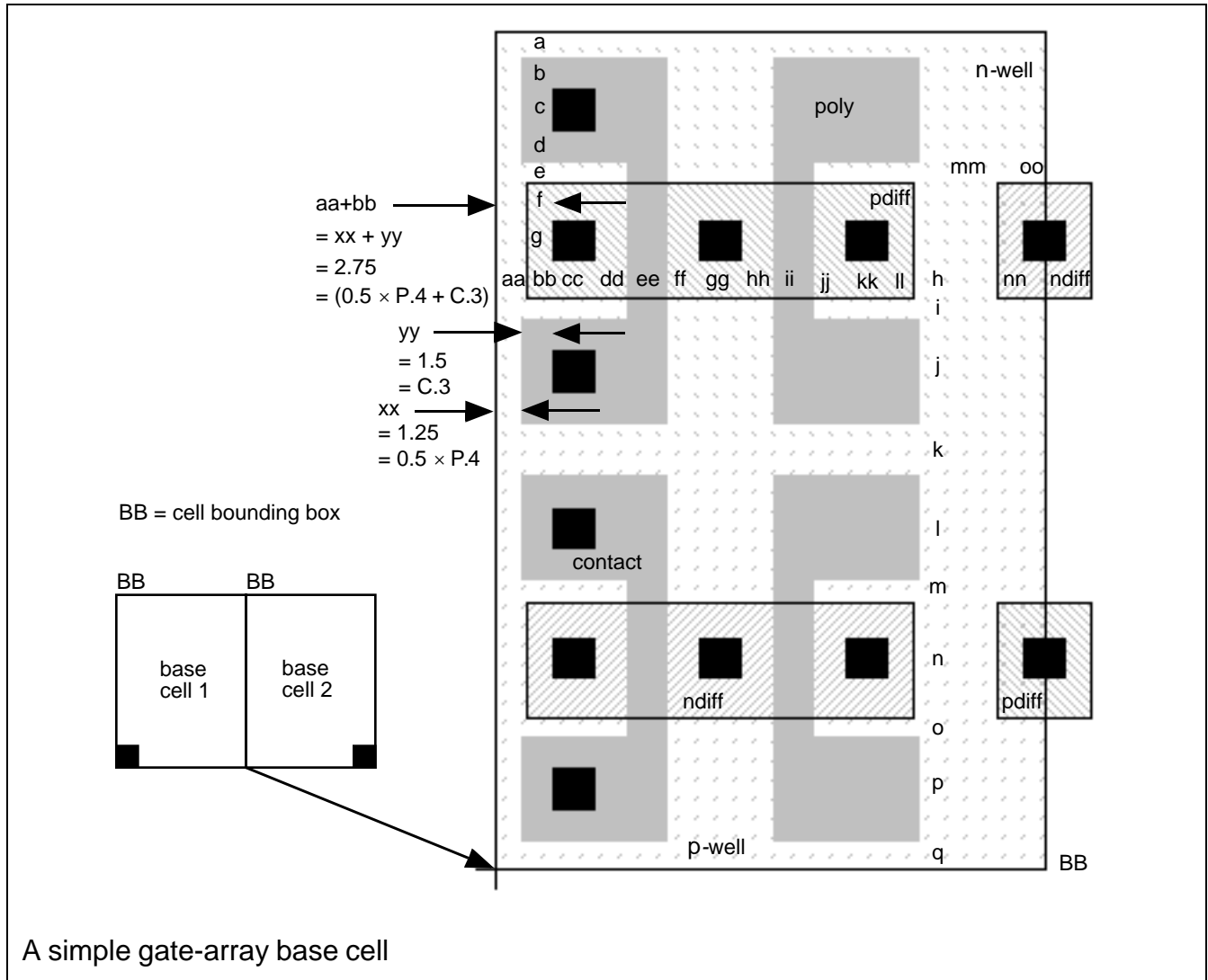- This is CBA I for 2LM (CBA II is intended for 3LM and salicide proceses)




3.7 Standard-Cell Design


 


A D flip-flop standard cell

- **Performance-optimized library** • **Area-optimized library**
- Wide **power buses** and transistors for a performance-optimized cell
- **Double-entry cell** intended for a 2LM process and channel routing
- Five **connectors** run vertically through the cell on m2
- The extra short vertical metal line is an internal **crossover**
- **bounding box (BB)** • **abutment box (AB)** • **physical connector** • **abut**

 

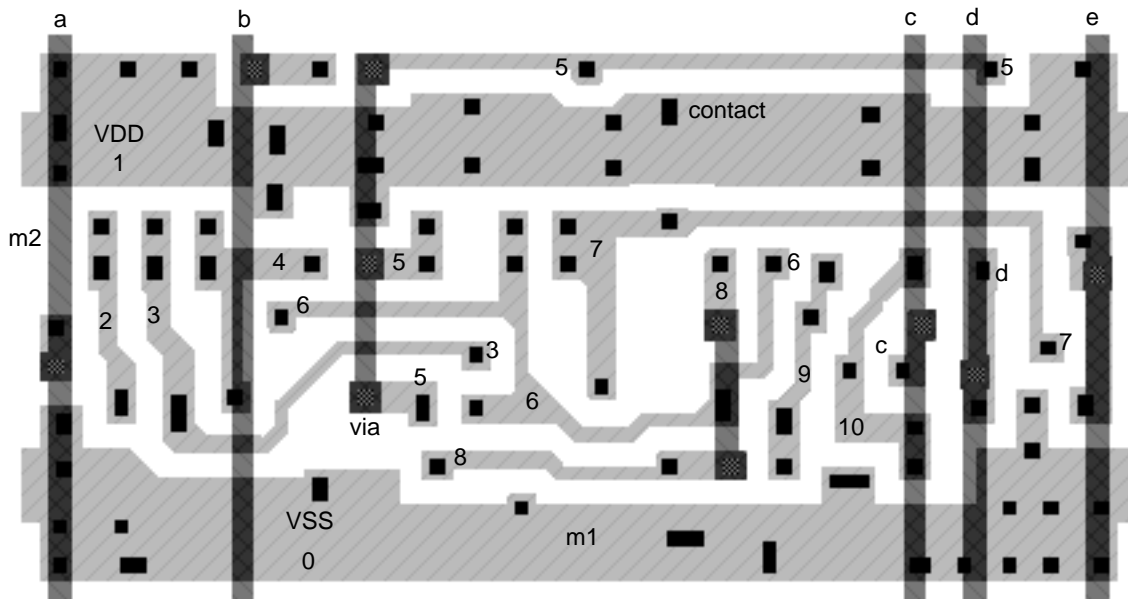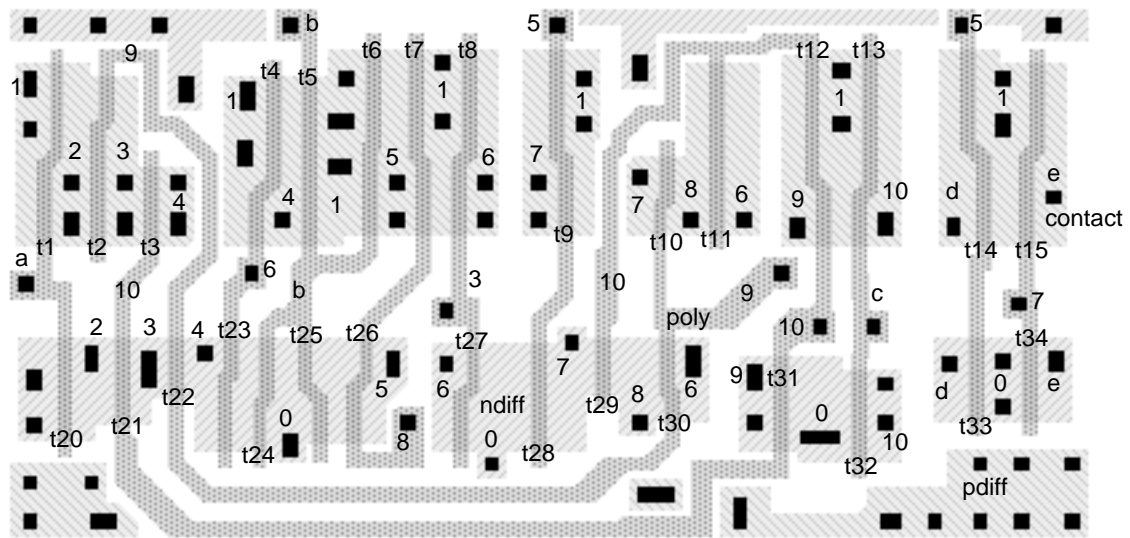A D flip-flop from a 1.0µm standard-cell library





D flip-flop

(Top) n-diffusion, p-diffusion, poly, contact (n-well and p-well are not shown)

(Bottom) m1, contact, m2, and via layers

3.8 Datapath-Cell Design

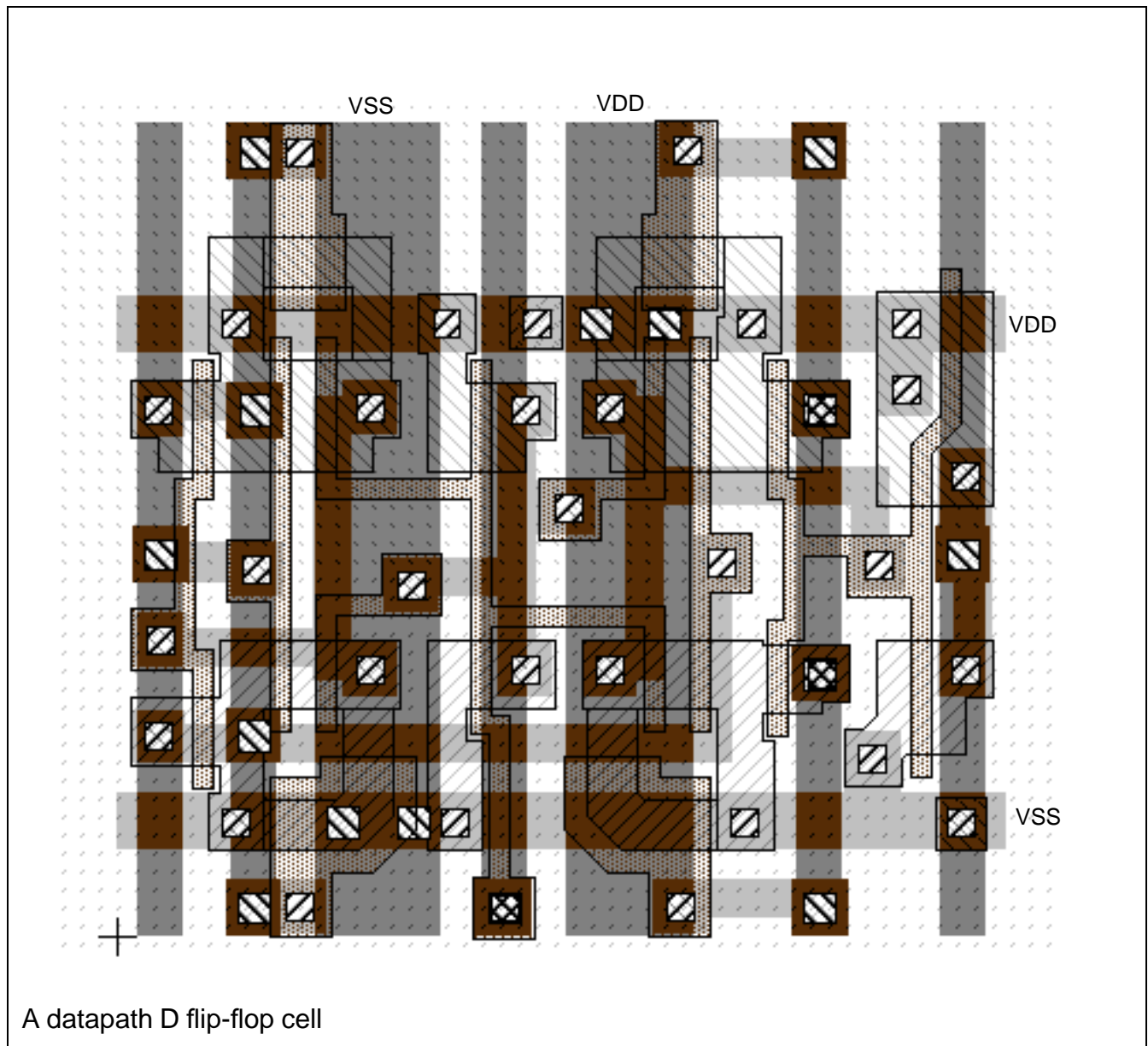

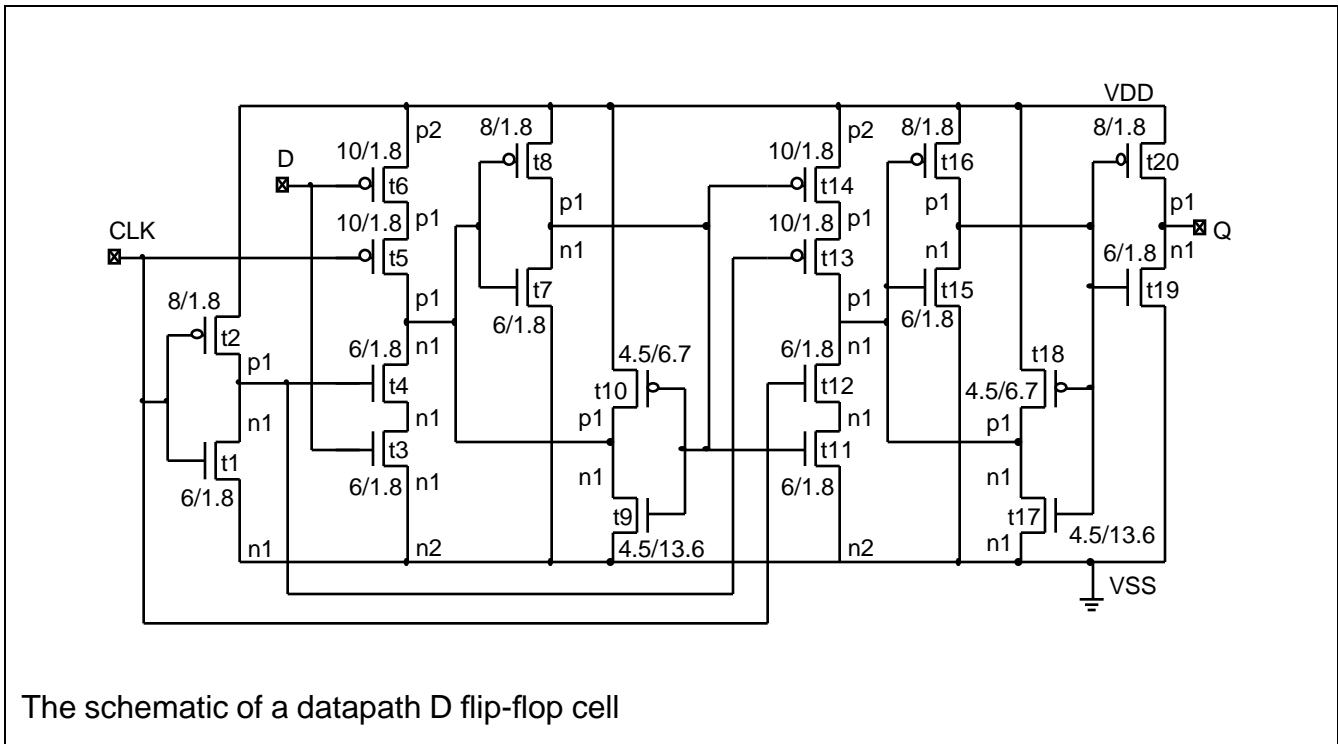

A narrow datapath

(a) Implemented in a two-level metal process

(b) Implemented in a three-level metal process

3.9 Summary

Key concepts:

- Tau, logical effort, and the prediction of delay
- Sizes of cells, and their drive strengths
- Cell importance
- The difference between gate-array macros, standard cells, and datapath cells

