

# SIMULATION

13

*Key terms and concepts:* Engineers used to prototype systems to check designs • Breadboarding is feasible for systems constructed from a few TTL parts • It is impractical for an ASIC • Instead engineers turn to **simulation**

## 13.1 Types of Simulation

*Key terms and concepts:* **simulation modes** (high-level to low-level simulation—high-level is more abstract, low-level more detailed): Behavioral simulation • Functional simulation • Static timing analysis • Gate-level simulation • Switch-level simulation • Transistor-level or circuit-level simulation

## 13.2 The Comparator/MUX Example

*Key terms and concepts:* using **input vectors** to test or **exercise** a behavioral model • simulation can only prove a design does not work; it cannot prove that hardware will work

```
// comp_mux.v                                         //1
module comp_mux(a, b, outp); input [2:0] a, b; output [2:0] outp; //2
function [2:0] compare; input [2:0] ina, inb; //3
begin if (ina <= inb) compare = ina; else compare = inb; end //4
endfunction                                         //5
assign outp = compare(a, b);                         //6
endmodule                                         //7

// testbench.v                                       //1
module comp_mux_testbench;                         //2
integer i, j;                                     //3
reg [2:0] x, y, smaller; wire [2:0] z;           //4
always @(x) $display("t      x y actual calculated"); //5
initial $monitor("%4g",$time,,x,,y,,z,,smaller); //6
initial $dumpvars; initial #1000 $finish;          //7
initial                                         //8
```

```

begin //9
  for (i = 0; i <= 7; i = i + 1) //10
    begin //11
      for (j = 0; j <= 7; j = j + 1) //12
        begin //13
          x = i; y = j; smaller = (x <= y) ? x : y; //14
          #1 if (z != smaller) $display("error"); //15
        end //16
      end //17
    end //18
  comp_mux v_1 (x, y, z); //19
endmodule //20

```

### 13.2.1 Structural Simulation

*Key terms and concepts:* logic synthesis produces a structural model from a behavioral model • reference model • derived model • **vector-based simulation** (or **dynamic simulation**)

```

`timescale 1ns / 10ps // comp_mux_o2.v //1
module comp_mux_o (a, b, outp); //2
  input [2:0] a; input [2:0] b; //3
  output [2:0] outp; //4
  supply1 VDD; supply0 VSS; //5
  mx21d1 b1_i1 (.i0(a[0]), .i1(b[0]), .s(b1_i6_zn), .z(outp[0])); //6
  oa03d1 b1_i2 (.a1(b1_i9_zn), .a2(a[2]), .b1(a[0]), .b2(a[1]), //7
    .c(b1_i4_zn), .zn(b1_i2_zn)); //8
  nd02d0 b1_i3 (.a1(a[1]), .a2(a[0]), .zn(b1_i3_zn)); //9
  nd02d0 b1_i4 (.a1(b[1]), .a2(b1_i3_zn), .zn(b1_i4_zn)); //10
  mx21d1 b1_i5 (.i0(a[1]), .i1(b[1]), .s(b1_i6_zn), .z(outp[1])); //11
  oa04d1 b1_i6 (.a1(b[2]), .a2(b1_i7_zn), .b(b1_i2_zn), //12
    .zn(b1_i6_zn)); //13
  in0ld0 b1_i7 (.i(a[2]), .zn(b1_i7_zn)); //14
  an02d1 b1_i8 (.a1(b[2]), .a2(a[2]), .z(outp[2])); //15
  in0ld0 b1_i9 (.i(b[2]), .zn(b1_i9_zn)); //16
endmodule //17

`timescale 1 ns / 10 ps //1
module mx21d1 (z, i0, i1, s); input i0, i1, s; output z; //2
  not G3(N3, s); //3
  and G4(N4, i0, N3), G5(N5, s, i1), G6(N6, i0, i1); //4
  or G7(z, N4, N5, N6); //5
specify //6
  (i0*>z) = (0.279:0.504:0.900, 0.276:0.498:0.890); //7

```

```

(i1*>z) = (0.248:0.448:0.800, 0.264:0.476:0.850);           //8
(s*>z)  = (0.285:0.515:0.920, 0.298:0.538:0.960);           //9
endspecify                                                 //10
endmodule                                                 //11

`timescale 1 ps / 1 ps // comp_mux_testbench2.v                //1
module comp_mux_testbench2;                                     //2
  integer i, j; integer error;                                //3
  reg [2:0] x, y, smaller; wire [2:0] z, ref;               //4
  always @(x) $display("t      x y derived reference");       //5
  // initial $monitor("%8.2f",$time/1e3,,x,,y,,z,,ref);        //6
  initial $dumpvars;                                         //7
  initial begin                                            //8
    error = 0; #1e6 $display("%4g", error, " errors");         //9
    $finish;                                                 //10
  end                                                       //11
  initial begin                                            //12
    for (i = 0; i <= 7; i = i + 1)begin                         //13
      for (j = 0; j <= 7; j = j + 1)begin                         //14
        x = i; y = j; #10e3;
        $display("%8.2f",$time/1e3,,x,,y,,z,,ref);             //15
        if (z != ref)                                         //16
          begin $display("error"); error = error + 1;end           //17
      end                                                 //18
    end                                                       //19
  end                                                       //20
end                                                       //21
comp_mux_o v_1 (x, y, z); // comp_mux_o2.v                  //22
reference v_2 (x, y, ref);                                    //23
endmodule                                                 //24

// reference.v                                              //1
module reference(a, b, outp);                            //2
  input [2:0] a, b;output [2:0] outp;                   //3
  assign outp = (a <= b) ? a : b; // different from comp_mux //4
endmodule                                                 //5

```

### 13.2.2 Static Timing Analysis

*Key terms and concepts:* “What is the longest delay in my circuit?” • timing analysis finds the critical path and its delay • timing analysis does not find the input vectors that activate the critical path • **Boolean relations** • **false paths** • a timing-analyzer is more logic calculator than logic simulator

### 13.2.3 Gate-Level Simulation

*Key terms and concepts:* differences between functional simulation, timing analysis, and gate-level simulation

```
# The calibration was done at Vdd=4.65V, Vss=0.1V, T=70 degrees C
Time = 0:0 [0 ns]
      a = 'D6 [0] (input)(display)
      b = 'D7 [0] (input)(display)
      outp = 'Buuu ('Du) [0] (display)
      outp --> 'Bluu ('Du) [.47]
      outp --> 'B1lu ('Du) [.97]
      outp --> 'D6 [4.08]
      a --> 'D7 [10]
      b --> 'D6 [10]
      outp --> 'D7 [10.97]
      outp --> 'D6 [14.15]
Time = 0:0 +20ns [20 ns]
```

### 13.2.4 Net Capacitance

*Key terms and concepts:* **net capacitance** (interconnect capacitance or wire capacitance) • **wire-load model, wire-delay model, or interconnect model**

```
@nodes
a R10 W1; a[2] a[1] a[0]
b R10 W1; b[2] b[1] b[0]
outp R10 W1; outp[2] outp[1] outp[0]
@data
      .00          a -> 'D6
      .00          b -> 'D7
      .00          outp -> 'Du
      .53          outp -> 'Du
      .93          outp -> 'Du
      4.42         outp -> 'D6
      10.00        a -> 'D7
      10.00        b -> 'D6
      11.03        outp -> 'D7
      14.43        outp -> 'D6
### END OF SIMULATION TIME = 20 ns
@end
```

## 13.3 Logic Systems

*Key terms and concepts:* **Digital simulation** • **logic values** (or **logic states**) from a **logic system** • A **two-value logic system** (or two-state logic system) has logic value '0' (**logic level 'zero'**) and a logic value '1' (**logic level 'one'**) • logic value 'X' (**unknown logic level**) or **unknown** • an unknown can **propagate** through a circuit • to model a three-state bus, we need a **high-impedance state** (logic level of 'zero' or 'one') but it is not being driven • A **four-value logic system**

### A four-value logic system

Logic state	Logic level	Logic value
0	zero	zero
1	one	one
X	zero or one	unknown
Z	zero, one, or neither	high impedance

### 13.3.1 Signal Resolution

*Key terms and concepts:* **signal-resolution function** • commutative and associative

**A resolution function  $R\{A, B\}$  that predicts the result of two drivers simultaneously attempting to drive signals with values A and B onto a bus**

$R\{A, B\}$	B=0	B=1	B=X	B=Z
A=0	0	X	X	0
A=1	X	1	X	1
A=X	X	X	X	X
A=Z	0	1	X	Z

### 13.3.2 Logic Strength

*Key terms and concepts:* n-channel transistors produce a logic level 'zero' (with a forcing strength) • p-channel transistors force a logic level 'one' • An n-channel transistor provides a

weak logic level 'one', a **resistive 'one'**, with **resistive strength** • **high impedance** • **Verilog logic system** • **VHDL signal resolution** using **VHDL signal-resolution functions**

### A 12-state logic system

Logic strength	Logic level		
	zero	unknown	one
<b>strong</b>	S0	SX	S1
<b>weak</b>	W0	WX	W1
<b>high impedance</b>	Z0	ZX	Z1
<b>unknown</b>	U0	UX	U1

### Verilog logic strengths

Logic strength	Strength number	Models	Abbreviation	
supply drive	7	power supply	supply	Su
strong drive	6	default gate and assign output strength	strong	St
pull drive	5	gate and assign output strength	pull	Pu
large capacitor	4	size of trireg net capacitor	large	La
weak drive	3	gate and assign output strength	weak	We
medium capacitor	2	size of trireg net capacitor	medium	Me
small capacitor	1	size of trireg net capacitor	small	Sm
high impedance	0	not applicable	highz	Hi

### The nine-value logic system, IEEE Std 1164-1993.

Logic state	Logic value	Logic state	Logic value
'0'	strong low	'X'	strong unknown
'1'	strong high	'W'	weak unknown
'L'	weak low	'Z'	high impedance
'H'	weak high	'-'	don't care
		'U'	uninitialized

```

function "and"(l,r : std_ulogic_vector) return std_ulogic_vector
is
    alias lv : std_ulogic_vector (1 to l'LENGTH) is l; --1
    alias rv : std_ulogic_vector (1 to r'LENGTH) is r; --2
    variable result : std_ulogic_vector (1 to l'LENGTH); --3

```

## 13.4 How Logic Simulation Works

*Key terms and concepts:* event-driven simulator • event • event queue or event list • evaluation • time step • interpreted-code simulator • compiled-code simulator • native-code simulator • evaluation list • simulation cycle, or an event–evaluation cycle • time wheel

```
model nd01d1 (a, b, zn)
function (a, b) !(a & b); function end
model end
```

nand nd01d1(a2, b3, r7)

```

struct Event {
    event_ptr fwd_link, back_link; /* event list */
    event_ptr node_link; /* list of node events */
    node_ptr event_node; /* node for the event */
    node_ptr cause; /* node causing event */
    port_ptr port; /* port which caused this event */
    long event_time; /* event time, in units of delta */
    char new_value; /* new value: '1' '0' etc. */
};


```

### 13.4.1 VHDL Simulation Cycle

*Key terms and concepts:* **simulation cycle** • elaboration • a **delta cycle** takes **delta time** • **time step** • postponed processes

A VHDL simulation cycle consists of the following steps:

1. The current time,  $t_c$  is set equal to  $t_n$ .
2. Each active signal in the model is updated and events may occur as a result.
3. For each process P, if P is currently sensitive to a signal S, and an event has occurred on signal S in this simulation cycle, then process P resumes.
4. Each resumed process is executed until it suspends.
5. The time of the next simulation cycle,  $t_n$ , is set to the earliest of:
  - a. the next time at which a driver becomes active or
  - b. the next time at which a process resumes
6. If  $t_n = t_c$ , then the next simulation cycle is a delta cycle.
7. Simulation is complete when we run out of time ( $t_n = \text{TIME}'\text{HIGH}$ ) and there are no active drivers or process resumptions at  $t_n$

### 13.4.2 Delay

*Key terms and concepts:* **delay mechanism** • **transport delay** is characteristic of wires and transmission lines • **Inertial delay** models the behavior of logic cells • a logic cell will not transmit a pulse that is shorter than the switching time of the circuit, the default **pulse-rejection limit**

```

Op <= Ip after 10 ns;                                --1
Op <= inertial Ip after 10 ns;                      --2
Op <= reject 10 ns inertial Ip after 10 ns;          --3
-- Assignments using transport delay:                  --1
Op <= transport Ip after 10 ns;                      --2
Op <= transport Ip after 10 ns, not Ip after 20 ns;   --3

```

---

```
-- Their equivalent assignments: --4
Op <= reject 0 ns inertial Ip after 10 ns; --5
Op <= reject 0 ns inertial Ip after 10 ns, not Ip after 10 ns; --6
```

## 13.5 Cell Models

*Key terms and concepts:* delay model • power model • timing model • primitive model

There are several different kinds of logic cell models:

- Primitive models, produced by the ASIC library company and describe the function and properties of logic cells using primitive functions.
- Verilog and VHDL models produced by an ASIC library company from the primitive models.
- Proprietary models produced by library companies that describe small logic cells or functions such as microprocessors.

### 13.5.1 Primitive Models

*Key terms and concepts:* **primitive model** • a designer does not normally see a primitive model; it may only be used by an ASIC library company to generate other models

```
Function
(timingModel = oneOf("ism","pr"); powerModel = oneOf("pin"); )
Rec
Logic = Function (A1; A2; )Rec ZN = not (A1 AND A2); End; End;
miscInfo = Rec Title = "2-Input NAND, 1X Drive"; freq_fact = 0.5;
tml = "nd02d1 nand 2 * zn a1 a2";
MaxParallel = 1; Transistors = 4; power = 0.179018;
Width = 4.2; Height = 12.6; productName = "stdcell35"; libraryName =
"cb35sc"; End;
Pin = Rec
A1 = Rec input; cap = 0.010; doc = "Data Input"; End;
A2 = Rec input; cap = 0.010; doc = "Data Input"; End;
ZN = Rec output; cap = 0.009; doc = "Data Output"; End; End;
Symbol = Select
timingModel
On pr Do Rec
tA1D_fr = |( Rec prop = 0.078; ramp = 2.749; End);
tA1D_rf = |( Rec prop = 0.047; ramp = 2.506; End);
tA2D_fr = |( Rec prop = 0.063; ramp = 2.750; End);
tA2D_rf = |( Rec prop = 0.052; ramp = 2.507; End);
On ism Do Rec
```

```
tA1D_fr = |( Rec A0 = 0.0015; dA = 0.0789; D0 = -0.2828;
dD = 4.6642; B = 0.6879; Z = 0.5630; End );
tA1D_rf = |( Rec A0 = 0.0185; dA = 0.0477; D0 = -0.1380;
dD = 4.0678; B = 0.5329; Z = 0.3785; End );
tA2D_fr = |( Rec A0 = 0.0079; dA = 0.0462; D0 = -0.2819;
dD = 4.6646; B = 0.6856; Z = 0.5282; End );
tA2D_rf = |( Rec A0 = 0.0060; dA = 0.0464; D0 = -0.1408;
dD = 4.0731; B = 0.6152; Z = 0.4064; End ); End; End;
Delay = |( Rec from = pin.A1; to = pin.ZN;
edges = Rec fr = Symbol.tA1D_fr; rf = Symbol.tA1D_rf; End; End, Rec
from = pin.A2; to = pin.ZN; edges = Rec fr = Symbol.tA2D_fr; rf =
Symbol.tA2D_rf; End; End );
MaxRampTime = |( Rec check = pin.A1; riseTime = 3.000; fallTime =
3.000; End, Rec check = pin.A2; riseTime = 3.000; fallTime =
3.000; End, Rec check = pin.ZN; riseTime = 3.000; fallTime =
3.000; End );
DynamicPower = |( Rec rise = { ZN }; val = 0.003; End); End; End
```

### 13.5.2 Synopsys Models

*Key terms and concepts:* **vendor models** • each logic cell is part of a file that also contains wire-load models and other characterization information for the cell library • not all of the information from a primitive model is present in a vendor model

```
cell (nd02d1) {
/* title : 2-Input NAND, 1X Drive */
/* pmd checksum : 'HBA7EB26C */
area : 1;
pin(a1) { direction : input; capacitance : 0.088;
fanout_load : 0.088; }
pin(a2) { direction : input; capacitance : 0.087;
fanout_load : 0.087; }
pin(zn) { direction : output; max_fanout : 1.786;
max_transition : 3; function : "(a1 a2)'";
timing() {
    timing_sense : "negative_unate"
    intrinsic_rise : 0.24 intrinsic_fall : 0.17
    rise_resistance : 1.68 fall_resistance : 1.13
    related_pin : "a1" }
timing() { timing_sense : "negative_unate"
    intrinsic_rise : 0.32 intrinsic_fall : 0.18
    rise_resistance : 1.68 fall_resistance : 1.13
```

```

    related_pin : "a2"
} } /* end of cell */

```

### 13.5.3 Verilog Models

*Key terms and concepts:* Verilog timing models • SDF file contains back-annotation timing delays • delays are calculated by a **delay calculator** • \$sdf\_annotate performs back-annotation • **golden simulator**

```

`celldefine                                //1
`delay_mode_path                           //2
`suppress_faults                          //3
`enable_portfaults                      //4
`timescale 1 ns / 1 ps                   //5
module in0ld1 (zn, i); input i; output zn; not G2(zn, i);           //6
specify specparam                         //7
InCap$i = 0.060, OutCap$zn = 0.038, MaxLoad$zn = 1.538,             //8
R_Ramp$i$zn = 0.542:0.980:1.750, F_Ramp$i$zn = 0.605:1.092:1.950; //9
specparam cell_count = 1.000000; specparam Transistors = 4 ;          //10
specparam Power = 1.400000; specparam MaxLoadedRamp = 3 ;            //11
  (i => zn) = (0.031:0.056:0.100, 0.028:0.050:0.090);           //12
endspecify                                //13
endmodule                                 //14
`nosuppress_faults                      //15
`disable_portfaults                     //16
`endcelldefine                           //17

`timescale 1 ns / 1 ps                   //1
module SDF_b; reg A; in0ld1 i1 (B, A);           //2
initial begin A = 0; #5; A = 1; #5; A = 0; end      //3
initial $monitor("T=%6g",$realtime," A=",A," B=",B); //4
endmodule                                     //5

```

```

T=      0 A=0 B=x
T= 0.056 A=0 B=1
T=      5 A=1 B=1
T=  5.05 A=1 B=0
T=     10 A=0 B=0
T=10.056 A=0 B=1

```

```
(DELAYFILE
  (SDFVERSION "3.0") (DESIGN "SDF.v") (DATE "Aug-13-96")
  (VENDOR "MJSS") (PROGRAM "MJSS") (VERSION "v0")
  (DIVIDER .) (TIMESCALE 1 ns)
  (CELL (CELLTYPE "in0ld1")
    (INSTANCE SDF_b.i1)
    (DELAY (ABSOLUTE
      (IOPATH i zn (1.151:1.151:1.151) (1.363:1.363:1.363)))
    )))
)
`timescale 1 ns / 1 ps //1
module SDF_b; reg A; in0ld1 i1 (B, A); //2
initial begin //3
$sdff_annotation ("SDF_b.sdf", SDF_b, , "sdf_b.log", "minimum", , );
A = 0; #5; A = 1; #5; A = 0; end //5
initial $monitor("T=%6g",$realtime," A=",A," B=",B); //6
endmodule //7
```

Here is the output (from MTI V-System/Plus) including back-annotated timing:

```
T=      0 A=0 B=x
T= 1.151 A=0 B=1
T=      5 A=1 B=1
T= 6.363 A=1 B=0
T=     10 A=0 B=0
T=11.151 A=0 B=1
```

### 13.5.4 VHDL Models

*Key terms and concepts:* VHDL alone does not offer a standard way to perform back-annotation.

- VITAL

```
library IEEE; use IEEE.STD_LOGIC_1164.all;
library COMPASS_LIB; use COMPASS_LIB.COMPASS_ETC.all;
entity bknot is
  generic (derating : REAL := 1.0; Z1_cap : REAL := 0.000;
           INSTANCE_NAME : STRING := "bknot");
  port (Z2 : in Std_Logic; Z1 : out STD_LOGIC);
end bknot;
```

```

architecture bknot of bknot is
constant tplh_Z2_Z1 : TIME := (1.00 ns + (0.01 ns * Z1_Cap)) *
derating;
constant tphl_Z2_Z1 : TIME := (1.00 ns + (0.01 ns * Z1_Cap)) *
derating;
begin
  process(Z2)
    variable int_Z1 : Std_Logic := 'U';
    variable tplh_Z1, tphl_Z1, Z1_delay : time := 0 ns;
    variable CHANGED : BOOLEAN;
    begin
      int_Z1 := not (Z2);
      if Z2'EVENT then
        tplh_Z1 := tplh_Z2_Z1; tphl_Z1 := tphl_Z2_Z1;
      end if;
      Z1_delay := F_Delay(int_Z1, tplh_Z1, tphl_Z1);
      Z1 <= int_Z1 after Z1_delay;
    end process;
  end bknot;
configuration bknot_CON of bknot is for bknot end for;
end bknot_CON;

```

### 13.5.5 VITAL Models

*Key terms and concepts:* VITAL • VHDL Initiative Toward ASIC Libraries, IEEE Std 1076.4 [1995] • . sign-off quality ASIC libraries using an approved cell library and a golden simulator

```

library IEEE; use IEEE.STD_LOGIC_1164 all; --1
use IEEE.VITAL_timing all; use IEEE.VITAL_primitives all; --2
entity IN01D1 is --3
  generic ( --4
    tipd_I : VitalDelayType01 := (0 ns, 0 ns); --5
    tpd_I_ZN : VitalDelayType01 := (0 ns, 0 ns) );
  port ( --7
    I : in STD_LOGIC := 'U'; --8
    ZN : out STD_LOGIC := 'U' );
attribute VITAL_LEVEL0 of IN01D1 : entity is TRUE; --10
end IN01D1; --11
architecture IN01D1 of IN01D1 is --12
  attribute VITAL_LEVEL1 of IN01D1 : architecture is TRUE; --13
  signal I_ipd : STD_LOGIC := 'X'; --14
  begin --15
    WIREDelay:block
      begin VitalWireDelay(I_ipd, I, tipd_I);end block; --17

```

```

VITALbehavior : process (I_ipd) --18
variable ZN_zd : STD_LOGIC; --19
variable ZN_GlitchData : VitalGlitchDataType; --20
begin --21
ZN_zd := VitalINV(I_ipd); --22
VitalPathDelay01( --23
  OutSignal => ZN, --24
  OutSignalName => "ZN", --25
  OutTemp => ZN_zd, --26
  Paths => (0 => (I_ipd'LAST_EVENT, tpd_I_ZN, TRUE)), --27
  GlitchData => ZN_GlitchData, --28
  DefaultDelay => VitalZeroDelay01, --29
  Mode => OnEvent, --30
  MsgOn => FALSE, --31
  XOn => TRUE, --32
  MsgSeverity => ERROR);
end process; --34
end IN01D1; --35

library IEEE; use IEEE.STD_LOGIC_1164.all; --1
entity SDF is port ( A : in STD_LOGIC; B : out STD_LOGIC ); --2
end SDF; --3
architecture SDF of SDF is --4
component in01d1 port ( I : in STD_LOGIC; ZN : out STD_LOGIC ); --5
end component; --6
begin i1: in01d1 port map ( I => A, ZN => B );
end SDF; --8

library STD; use STD.TEXTIO.all; --1
library IEEE; use IEEE.STD_LOGIC_1164.all; --2
entity SDF_testbench is end SDF_testbench; --3
architecture SDF_testbench of SDF_testbench is --4
component SDF port ( A : in STD_LOGIC; B : out STD_LOGIC ); --5
end component; --6
signal A, B : STD_LOGIC := '0'; --7
begin --8
  SDF_b : SDF port map ( A => A, B => B ); --9
  process begin --10
    A <= '0'; wait for 5 ns; A <= '1';
    wait for 5 ns; A <= '0'; wait;
  end process; --13
  process (A, B) variable L: LINE; begin --14
    write(L, now, right, 10, TIME'(ps));
    write(L, STRING'" A=""); write(L, TO_BIT(A)); --15
    write(L, STRING'" B=""); write(L, TO_BIT(B)); --16
    writeline(output, L); --17
  end process;
end;

```

```

end process; --19
end SDF_testbench; --20

```

```

(DELAYFILE
  (SDFVERSION "3.0") (DESIGN "SDF.vhd") (DATE "Aug-13-96")
  (VENDOR "MJSS") (PROGRAM "MJSS") (VERSION "v0")
  (DIVIDER .) (TIMESCALE 1 ns)
  (CELL (CELLTYPE "in01d1")
    (INSTANCE i1)
    (DELAY (ABSOLUTE
      (IOPATH i zn (1.151:1.151:1.151) (1.363:1.363:1.363))
      (PORT i (0.021:0.021:0.021) (0.025:0.025:0.025)))
    )))
  )
)
)

```

```

<msmith/MTI/vital> vsim -c -sdfmax /sdf_b=SDF_b.sdf sdf_testbench
...
#      0 ps A=0 B=0
#      0 ps A=0 B=0
#  1176 ps A=0 B=1
#  5000 ps A=1 B=1
#  6384 ps A=1 B=0
# 10000 ps A=0 B=0
# 11176 ps A=0 B=1

```

### 13.5.6 SDF in Simulation

*Key terms and concepts:* SDF is also used to describe forward-annotation of timing constraints from logic synthesis

```

(DELAYFILE
  (SDFVERSION "1.0")
  (DESIGN "halfgate ASIC_u")
  (DATE "Aug-13-96")
  (VENDOR "Compass")
  (PROGRAM "HDL Asst")
  (VERSION "v9r1.2")
  (DIVIDER .)
  (TIMESCALE 1 ns)
)

```

```
(CELL (CELLTYPE "in01d0")
  (INSTANCE v_1.B1_i1)
  (DELAY (ABSOLUTE
    (IOPATH I ZN (1.151:1.151:1.151) (1.363:1.363:1.363)))
  ))
)
(CELL (CELLTYPE "pc5o06")
  (INSTANCE u1_2)
  (DELAY (ABSOLUTE
    (IOPATH I PAD (1.216:1.216:1.216) (1.249:1.249:1.249)))
  ))
)
(CELL (CELLTYPE "pc5d01r")
  (INSTANCE u0_2)
  (DELAY (ABSOLUTE
    (IOPATH PAD CIN (.169:.169:.169) (.199:.199:.199)))
  ))
)
)

(DELAYFILE
  ...
  (PROCESS "FAST-FAST")
  (TEMPERATURE 0:55:100)
  (TIMESCALE 100ps)
(CELL (CELLTYPE "CHIP")
  (INSTANCE TOP)
  (DELAY (ABSOLUTE
    (INTERCONNECT A.INV8.OUT B.DFF1.Q (:0.6:) (:0.6:))
  )))
))

( INSTANCE B.DFF1)
(DELAY (ABSOLUTE
  (IOPATH (POSEDGE CLK) Q (12:14:15) (11:13:15)))))

(DELAYFILE
(DESIGN "MYDESIGN")
(DATE "26 AUG 1996")
(VENDOR "ASICs_INC")
(PROGRAM "SDF_GEN")
(VERSION "3.0")
(DIVIDER .)
```

```
(VOLTAGE 3.6:3.3:3.0)
(PROCESS "-3.0:0.0:3.0")
(TEMPERATURE 0.0:25.0:115.0)
(TIMESCALE )
(CELL
  (CELLTYPE "AOI221")
  (INSTANCE X0)
  (DELAY (ABSOLUTE
    (IOPATH A1 Y (1.11:1.42:2.47) (1.39:1.78:3.19))
    (IOPATH A2 Y (0.97:1.30:2.34) (1.53:1.94:3.50))
    (IOPATH B1 Y (1.26:1.59:2.72) (1.52:2.01:3.79))
    (IOPATH B2 Y (1.10:1.45:2.56) (1.66:2.18:4.10))
    (IOPATH C1 Y (0.79:1.04:1.91) (1.36:1.62:2.61)))
  ))))
```

## 13.6 Delay Models

*Key terms and concepts:* timing model describes delays outside logic cells • delay model describes delays inside logic cells • **pin-to-pin delay** is a delay between an input pin and an output pin of a logic cell • **pin delay** is a delay lumped to a certain pin of a logic cell (usually an input) • **net delay** or **wire delay** is a delay outside a logic cell • **prop-ramp delay model**

```
specify specparam //1
InCap$i = 0.060, OutCap$zn = 0.038, MaxLoad$zn = 1.538, //2
R_Ramp$i$zn = 0.542:0.980:1.750, F_Ramp$i$zn = 0.605:1.092:1.950; //3
specparam cell_count = 1.000000; specparam Transistors = 4 ; //4
specparam Power = 1.400000; specparam MaxLoadedRamp = 3 ; //5
(i=>zn)=(0.031:0.056:0.100, 0.028:0.050:0.090); //6
```

### 13.6.1 Using a Library Data Book

*Key terms and concepts:* **area-optimized library** (small) • **performance-optimized library** (fast)

#### Input capacitances for an inverter family (pF)

Library	inv1	invh	invs	inv8	inv12
Area	0.034	0.067	0.133	0.265	0.397
Performance	0.145	0.292	0.584	1.169	1.753

**Delay information for a 2:1 MUX**

From input	To output	Propagation delay			
		Extrinsic/ nspF <sup>-1</sup>	Area Intrinsic / ns	Performance Extrinsic / ns	Intrinsic / ns
D0\	Z\	2.10	1.42	0.5	0.8
D0/	Z/	3.66	1.23	0.68	0.70
D1\	Z\	2.10	1.42	0.50	0.80
D1/	Z/	3.66	1.23	0.68	0.70
SD\	Z\	2.10	1.42	0.50	0.80
SD\	Z/	3.66	1.09	0.70	0.73
SD/	Z\	2.10	2.09	0.5	1.09
SD/	Z/	3.66	1.23	0.68	0.70

**Process derating factors**

Process	Derating factor	Temperature and voltage derating factors					
		Supply voltage					
Slow	1.31	Tempera-ture/°C	4.5V	4.75V	5.00V	5.25V	5.50V
			-40	0.77	0.73	0.68	0.64
Nominal	1.0	0	1.00	0.93	0.87	0.82	0.78
Fast	0.75	25	1.14	1.07	1.00	0.94	0.90
		85	1.50	1.40	1.33	1.26	1.20
		100	1.60	1.49	1.41	1.34	1.28
		125	1.76	1.65	1.56	1.47	1.41

### 13.6.2 Input-Slope Delay Model

*Key terms and concepts:* submicron technologies must account for the effects of the rise (and fall) time of the input waveforms to a logic cell • nonlinear delay model

The input-slope model predicts delay in the fast-ramp region,  $D_{ISM}(50\%, FR)$ , as follows (0.5 trip points):

$$\begin{aligned}
 D_{ISM} & (50\%, FR) \\
 & = A_0 + D_0 C_L + 0.5 O_R = A_0 + D_0 C_L + d_A/2 + d_D C_L/2 \\
 & = 0.0015 + 0.5 \times 0.0789 + (-0.2828 + 0.5 \times 4.6642) C_L \\
 & = 0.041 + 2.05 C_L
 \end{aligned}$$

### 13.6.3 Limitations of Logic Simulation

*Key terms and concepts:* pin-to-pin delay model • timing information for most gate-level simulators is calculated once, before simulation • **state-dependent timing**

#### Switching characteristics of a two-input NAND gate

Symbol	Parameter	Fanout					
		FO = 0 /ns	FO = 1 /ns	FO = 2 /ns	FO = 4 /ns	FO = 8 /ns	K /nspF <sup>-1</sup>
$t_{PLH}$	Propagation delay, A to X	0.25	0.35	0.45	0.65	1.05	1.25
$t_{PHL}$	Propagation delay, B to X	0.17	0.24	0.30	0.42	0.68	0.79
$t_r$	Output rise time, X	1.01	1.28	1.56	2.10	3.19	3.40
$t_f$	Output fall time, X	0.54	0.69	0.84	1.13	1.71	1.83

### Switching characteristics of a half adder

Symbol	Parameter	Fanout					
		FO = 0 /ns	FO = 1 /ns	FO = 2 /ns	FO = 4 /ns	FO = 8 /ns	K /ns $\mu$ F $^{-1}$
$t_{PLH}$	Delay, A to S (B = '0')	0.58	0.68	0.78	0.98	1.38	1.25
$t_{PHL}$	Delay, A to S (B = '1')	0.93	0.97	1.00	1.08	1.24	0.48
$t_{PLH}$	Delay, B to S (B = '0')	0.89	0.99	1.09	1.29	1.69	1.25
$t_{PHL}$	Delay, B to S (B = '1')	1.00	1.04	1.08	1.15	1.31	0.48
$t_{PLH}$	Delay, A to CO	0.43	0.53	0.63	0.83	1.23	1.25
$t_{PHL}$	Delay, A to CO	0.59	0.63	0.67	0.75	0.90	0.48
$t_r$	Output rise time, X	1.01	1.28	1.56	2.10	3.19	3.40
$t_f$	Output fall time, X	0.54	0.69	0.84	1.13	1.71	1.83

## 13.7 Static Timing Analysis

*Key terms and concepts:* static timing analysis • pipelining • critical path

```

Instance name      in pin-->out pin      tr      total      incr      cell
-----
END_OF_PATH
outp_2_
OUT1           : D--->PAD          R      27.26
I_1_CM8        : S11--->Y         R      27.26    7.55      OUTBUF
I_2_CM8        : S11--->Y         R      19.71    4.40      CM8
I_3_CM8        : S11--->Y         R      15.31    5.20      CM8
IN1            : PAD--->Y         R      10.11    4.80      CM8
a_2_
BEGIN_OF_PATH

// comp_mux_rrr.v                                         //1
module comp_mux_rrr(a, b, clock, outp);                //2
input [2:0] a, b; output [2:0] outp; input clock;        //3
reg [2:0] a_r, a_rr, b_r, b_rr, outp; reg sel_r;       //4
wire sel = ( a_r <= b_r ) ? 0 : 1;                      //5
always @ (posedge clock) begin a_r <= a; b_r <= b; end    //6
always @ (posedge clock) begin a_rr <= a_r; b_rr <= b_r; end //7
always @ (posedge clock) outp <= sel_r ? b_rr : a_rr;     //8
always @ (posedge clock) sel_r <= sel;                   //9
endmodule                                              //10

-----INPAD to SETUP longest path-----
Rise delay, Worst case
Instance name      in pin-->out pin      tr      total      incr      cell
-----
```

```

END_OF_PATH
D.a_r_ff_b2          R      4.52    0.00    DF1
INBUF_24             : PAD--->Y   R      4.52    4.52    INBUF
a_2_                 R      0.00    0.00
BEGIN_OF_PATH

```

-----CLOCK to SETUP longest path-----  
Rise delay, Worst case

Instance name	in pin-->out pin	tr	total	incr	cell
END_OF_PATH					
D.sel_r_ff		R	9.99	0.00	DF1
I_1_CM8	: S10--->Y	R	9.99	0.00	CM8
I_3_CM8	: S00--->Y	R	9.99	4.40	CM8
a_r_ff_b1	: CLK--->Q	R	5.60	5.60	DF1
BEGIN_OF_PATH					

-----CLOCK to OUTPAD longest path-----  
Rise delay, Worst case

Instance name	in pin-->out pin	tr	total	incr	cell
END_OF_PATH					
outp_2_		R	11.95		
OUTBUF_31	: D--->PAD	R	11.95	7.55	OUTBUF
outp_ff_b2	: CLK--->Q	R	4.40	4.40	DF1
BEGIN_OF_PATH					

A timing analyzer examines the following types of paths:

1. An **entry path** (or input-to-D path) to a pipelined design. The longest **entry delay** (or input-to-setup delay) is 4.52 ns.
2. A **stage path** (register-to-register path or clock-to-D path) in a pipeline stage. The longest **stage delay** (clock-to-D delay) is 9.99 ns.
3. An **exit path** (clock-to-output path) from the pipeline. The longest **exit delay** (clock-to-output delay) is 11.95 ns.

### 13.7.1 Hold Time

*Key terms and concepts:* Hold-time problems occur if there is clock skew between adjacent flip-flops • To check for hold-time violations we find the clock skew for each clock-to-D path

```

timer> shortest
1st shortest path to all endpins
Rank Total Start pin      First Net      End Net      End pin
  0    4.0 b_rr_ff_b1:CLK b_rr_1_      DEF_NET_48    outp_ff_b1:D
  1    4.1 a_rr_ff_b2:CLK a_rr_2_      DEF_NET_46    outp_ff_b2:D
... 8 similar lines omitted ...

```

### 13.7.2 Entry Delay

*Key terms and concepts:* Before we can measure clock skew, we need to analyze the entry delays, including the clock tree

### 13.7.3 Exit Delay

*Key terms and concepts:* exit delays (the longest path between clock-pad input and an output) • critical path and operating frequency

### 13.7.4 External Setup Time

*Key terms and concepts:* external set-up time • internal set-up time • clock delay

Each of the six chip data inputs must satisfy the following set-up equation:

$$t_{SU}(\text{external}) > t_{SU}(\text{internal}) - (\text{clock delay}) + (\text{data delay})$$

## 13.8 Formal Verification

*Key terms and concepts:* logic synthesis converts a behavioral model to a structural model • How do we know that the two are the same? • **formal verification** can prove they are equivalent

### 13.8.1 An Example

*Key terms and concepts:* **reference model** • **derived model** • (1) the HDL is parsed • (2) a **finite-state machine compiler** extracts the states • (3) a **proof generator** automatically generates formulas to be proved • (4) the **theorem prover** attempts to prove the formulas

```

entity Alarm is                                --1
  port(Clock, Key, Trip : in bit; Ring : out bit); --2
end Alarm;                                     --3

architecture RTL of Alarm is                  --1
  type States is (Armed, Off, Ringing); signal State : States; --2
begin                                         --3
  process (Clock) begin                      --4
    if Clock = '1' and Clock'EVENT then      --5
      case State is                         --6
        when Off => if Key = '1' then State <= Armed; end if; --7
        when Armed => if Key = '0' then State <= Off;           --8
          elsif Trip = '1' then State <= Ringing;                 --9
          end if;                                         --10
      end case;
    end if;
  end process;
end architecture;

```

```

    when Ringing => if Key = '0' then State <= Off; end if;          --11
  end case;                                                        --12
end if;                                                       --13
end process;                                                 --14
Ring <= '1' when State = Ringing else '0';                  --15
end RTL;                                                    --16

library cells; use cells.all; // ...contains logic cell models      --1
architecture Gates of Alarm is                                --2
component Inverter port(i : in BIT;z : out BIT) ; end component; --3
component NAnd2 port(a,b : in BIT;z : out BIT) ; end component; --4
component NAnd3 port(a,b,c : in BIT;z : out BIT) ; end component; --5
component DFF port(d,c : in BIT; q,qn : out BIT) ; end component; --6
signal State, NextState : BIT_VECTOR(1downto 0);           --7
signal s0, s1, s2, s3 : BIT;                                 --8
begin
  g2: Inverter port map ( i => State(0), z => s1 );        --10
  g3: NAnd2 port map ( a => s1, b => State(1), z => s2 );   --11
  g4: Inverter port map ( i => s2, z => Ring );            --12
  g5: NAnd2 port map ( a => State(1), b => Key, z => s0 );  --13
  g6: NAnd3 port map ( a => Trip, b => s1, c => Key, z => s3 ); --14
  g7: NAnd2 port map ( a => s0, b => s3, z => NextState(1) ); --15
  g8: Inverter port map ( i => Key, z => NextState(0) );     --16
  state_ff_b0: DFF port map
  ( d => NextState(0), c => Clock, q => State(0), qn => open ); --18
  state_ff_b1: DFF port map
  ( d => NextState(1), c => Clock, q => State(1), qn => open ); --19
end Gates;                                              --21

```

### 13.8.2 Understanding Formal Verification

*Key terms and concepts:* The **formulas** to be proved are generated as **proof statements** • An **axiom** is an explicit or implicit fact (signal of type `BIT` may only be '`0`' and '`1`') • An **assertion** is derived from a statement placed in the HDL code • **implication** • **equivalence**

```
assert Key /= '1' or Trip /= '1' or NextState = Ringing
report "Alarm on and tripped but not ringing";
```

### Implication and equivalence

A	B	A	B	A	B
F	F	T		T	
F	T	T		F	
T	F	F		F	
T	T	T		T	

### 13.8.3 Adding an Assertion

*Key terms and concepts:* “The axioms of the reference model do not imply that the assertions of the reference model imply the assertions of the derived model.” Translation: “These two architectures differ in some way.”

```
<E> Assertion may be violated
SEVERITY: ERROR
REPORT: Alarm on and tripped but not ringing
FILE: .../alarm-rtl3.vhdl
FSM: alarm-rtl3
STATEMENT or DECLARATION: line8
.../alarm-rtl3.vhdl (line 8)
Context of the message is:
(key And trip And memoryofdriver__state(0))
```

```
case State is
    when Off => if Key = '1' then State <= Armed; end if; --1
    when Armed => if Key = '0' then State <= Off; --2
        elsif Trip = '1' then State <= Ringing; --3
        end if; --4
    when Ringing => if Key = '0' then State <= Off; end if; --5
end case; --6
--7
```

Prove (Axiom\_ref => (Assert\_ref => Assert\_der))

Formula is NOT VALID

But is VALID under Assert Context of alarm-rtl3

### 13.8.4 Completing a Proof

```

...
case State is
    when Off =>           if Key = '1' then
        if Trip = '1' then NextState <= Ringing;
        else NextState <= Armed;
        end if;
        end if;
    when Armed => if Key = '0' then NextState <= Off;
        elsif Trip = '1' then NextState <= Ringing;
        end if;
    when Ringing => if Key = '0' then NextState <= Off; end if;
end case;
...

```

## 13.9 Switch-Level Simulation

*Key terms and concepts:* The **switch-level simulator** is a more detailed level of simulation than we have discussed so far • Example: a true single-phase flip-flop using true single-phase clocking (TSPC)

## 13.10 Transistor-Level Simulation

*Key terms and concepts:* **transistor-level simulation** or **circuit-level simulation** • **SPICE** (or **Spice, Simulation Program with Integrated Circuit Emphasis**) developed at UC Berkeley


### 13.10.1 A PSpice Example

*Key terms and concepts:* **PSpice input deck**

```

OB September 5, 1996 17:27
.TRAN/OP 1ns 20ns
.PROBE
cl output Ground 10pF
VIN input Ground PWL(0us 5V 10ns 5V 12ns 0V 20ns 0V)
VGround 0 Ground DC 0V
Vdd +5V 0 DC 5V
m1 output input Ground Ground NMOS W=100u L=2u

```

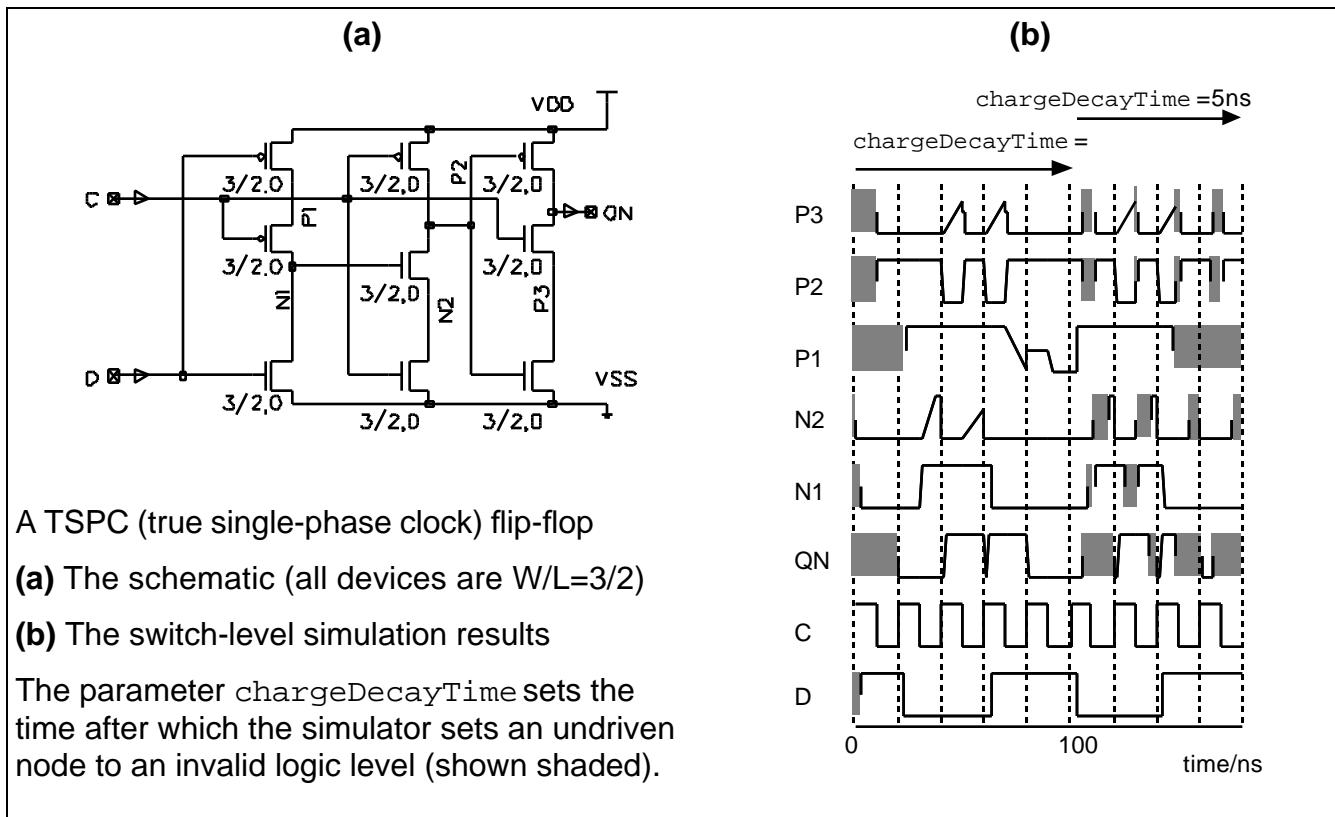

```
m2 output input +5V +5V PMOS W=200u L=2u
.model nmos nmos level=2 vto=0.78 tox=400e-10 nsub=8.0e15 xj=-0.15e-6
+ ld=0.20e-6 uo=650 ucrit=0.62e5 uexp=0.125 vmax=5.1e4 neff=4.0
+ delta=1.4 rsh=37 cgso=2.95e-10 cgdo=2.95e-10 cj=195e-6 cjsw=500e-12
+ mj=0.76 mjsw=0.30 pb=0.80
.model pmos pmos level=2 vto=-0.8 tox=400e-10 nsub=6.0e15 xj=-0.05e-6
+ ld=0.20e-6 uo=255 ucrit=0.86e5 uexp=0.29 vmax=3.0e4 neff=2.65
+ delta=1 rsh=125 cgso=2.65e-10 cgdo=2.65e-10 cj=250e-6 cjsw=350e-12
+ mj=0.535 mjsw=0.34 pb=0.80
.end
```

**13.10.2 SPICE Models**

*Key terms and concepts:* SPICE parameters • LEVEL=3 parameters

### SPICE transistor model parameters (LEVEL=3)

param- eter	n-ch. value	p-ch. value	Units	Explanation
CGBO	4.0E-10	3.8E-10	Fm <sup>-1</sup>	Gate–bulk overlap capacitance (CGBoh, not CGBzero)
CGDO	3.0E-10	2.4E-10	Fm <sup>-1</sup>	Gate–drain overlap capacitance (CGDoh, not CGDzero)
CGSO	3.0E-10	2.4E-10	Fm <sup>-1</sup>	Gate–source overlap capacitance (CGSoh, not CGSzzero)
CJ	5.6E-4	9.3E-4	Fm <sup>-2</sup>	Junction area capacitance
CJSW	5E-11	2.9E-10	Fm <sup>-1</sup>	Junction sidewall capacitance
DELTA	0.7	0.29	m	Narrow-width factor for adjusting threshold voltage
ETA	3.7E-2	2.45E-2	1	Static-feedback factor for adjusting threshold voltage
GAMMA	0.6	0.47	V <sup>0.5</sup>	Body-effect factor
KAPPA	2.9E-2	8	V <sup>-1</sup>	Saturation-field factor (channel-length modulation)
KP	2E-4	4.9E-5	AV <sup>-2</sup>	Intrinsic transconductance ( $\mu C_{ox}$ , not $0.5\mu C_{ox}$ )
LD	5E-8	3.5E-8	m	Lateral diffusion into channel
LEVEL	3		none	Empirical model
MJ	0.56	0.47	1	Junction area exponent
MJSW	0.52	0.50	1	Junction sidewall exponent
NFS	6E11	6.5E11	cm <sup>-2</sup> V <sup>-1</sup>	Fast surface-state density
NSUB	1.4E17	8.5E16	cm <sup>-3</sup>	Bulk surface doping
PB	1	1	V	Junction area contact potential
PHI	0.7		V	Surface inversion potential
RSH	2		/ square	Sheet resistance of source and drain
THETA	0.27	0.29	V <sup>-1</sup>	Mobility-degradation factor
TOX	1E-8		m	Gate-oxide thickness
TPG	1	-1	none	Type of polysilicon gate
U0	550	135	cm <sup>2</sup> V <sup>-1</sup> s <sup>-1</sup>	Low-field bulk carrier mobility (Uzero, not Uoh)
XJ	0.2E-6		m	Junction depth
VMAX	2E5	2.5E5	ms <sup>-1</sup>	Saturated carrier velocity
VTO	0.65	-0.92	V	Zero-bias threshold voltage (VTzero, not VToh)

### PSpice parameters for process G5 (PSpice LEVEL=4)

```

.MODEL NM1 NMOS LEVEL=4
+ VFB=-0.7, LVFB=-4E-2, WVFB=5E-2
+ PHI=0.84, LPHI=0, WPHI=0
+ K1=0.78, LK1=-8E-4, WK1=-5E-2
+ K2=2.7E-2, LK2=5E-2, WK2=-3E-2
+ ETA=-2E-3, LETA=2E-02, WETA=-5E-3
+ MUZ=600, DL=0.2, DW=0.5
+ U0=0.33, LU0=0.1, WU0=-0.1
+ U1=3.3E-2, LU1=3E-2, WU1=-1E-2
+ X2MZ=9.7, LX2MZ=-6, WX2MZ=7
+ X2E=4.4E-4, LX2E=-3E-3, WX2E=9E-4
+ X3E=-5E-5, LX3E=-2E-3, WX3E=-1E-3
+ X2U0=-1E-2, LX2U0=-1E-3, WX2U0=5E-3
+ X2U1=-1E-3, LX2U1=1E-3, WX2U1=-7E-4
+ MUS=700, LMUS=-50, WMUS=7
+ X2MS=-6E-2, LX2MS=1, WX2MS=4
+ X3MS=9, LX3MS=2, WX3MS=-6
+ X3U1=9E-3, LX3U1=2E-4, WX3U1=-5E-3
+ TOX=1E-2, TEMP=25, VDD=5
+ CGDO=3E-10, CGSO=3E-10, CGBO=4E-10
+ XPART=1
+ N0=1, LN0=0, WN0=0
+ NB=0, LNB=0, WNB=0
+ ND=0, LND=0, WND=0
* n+ diffusion
+ RSH=2.1, CJ=3.5E-4, CJSW=2.9E-10
+ JS=1E-8, PB=0.8, PBSW=0.8
+ MJ=0.44, MJSW=0.26, WDF=0
*, DS=0

.MODEL PM1 PMOS LEVEL=4
+ VFB=-0.2, LVFB=4E-2, WVFB=-0.1
+ PHI=0.83, LPHI=0, WPHI=0
+ K1=0.35, LK1=-7E-02, WK1=0.2
+ K2=-4.5E-2, LK2=9E-3, WK2=4E-2
+ ETA=-1E-2, LETA=2E-2, WETA=-4E-4
+ MUZ=140, DL=0.2, DW=0.5
+ U0=0.2, LU0=6E-2, WU0=-6E-2
+ U1=1E-2, LU1=1E-2, WU1=7E-4
+ X2MZ=7, LX2MZ=-2, WX2MZ=1
+ X2E= 5E-5, LX2E=-1E-3, WX2E=-2E-4
+ X3E=8E-4, LX3E=-2E-4, WX3E=-1E-3
+ X2U0=9E-3, LX2U0=-2E-3, WX2U0=2E-3
+ X2U1=6E-4, LX2U1=5E-4, WX2U1=3E-4
+ MUS=150, LMUS=10, WMUS=4
+ X2MS=6, LX2MS=-0.7, WX2MS=2
+ X3MS=-1E-2, LX3MS=2, WX3MS=1
+ X3U1=-1E-3, LX3U1=-5E-4, WX3U1=1E-3
+ TOX=1E-2, TEMP=25, VDD=5
+ CGDO=2.4E-10, CGSO=2.4E-10, CGBO=3.8E-10
+ XPART=1
+ N0=1, LN0=0, WN0=0
+ NB=0, LNB=0, WNB=0
+ ND=0, LND=0, WND=0
* p+ diffusion
+ RSH=2, CJ=9.5E-4, CJSW=2.5E-10
+ JS=1E-8, PB=0.85, PBSW=0.85
+ MJ=0.44, MJSW=0.24, WDF=0
*, DS=0

```

## 13.11 Summary

**Key terms and concepts:** Behavioral simulation can only tell you only if your design will not work

- Prelayout simulation estimates of performance
- Finding a critical path is difficult because you need to construct input vectors to exercise the model
- Static timing analysis is the most widely used form of simulation
- Formal verification compares two different representations. It cannot prove your design will work
- Switch-level simulation can check the behavior of circuits that may not always have nodes that are driven or that use logic that is not complementary
- Transistor-level simulation is used when you need to know the analog, rather than the digital, behavior of circuit voltages
- trade-off in accuracy against run time

