 



Finite State Machines



Handouts: Lecture Slides, PS4, Lab3


From Last Time...

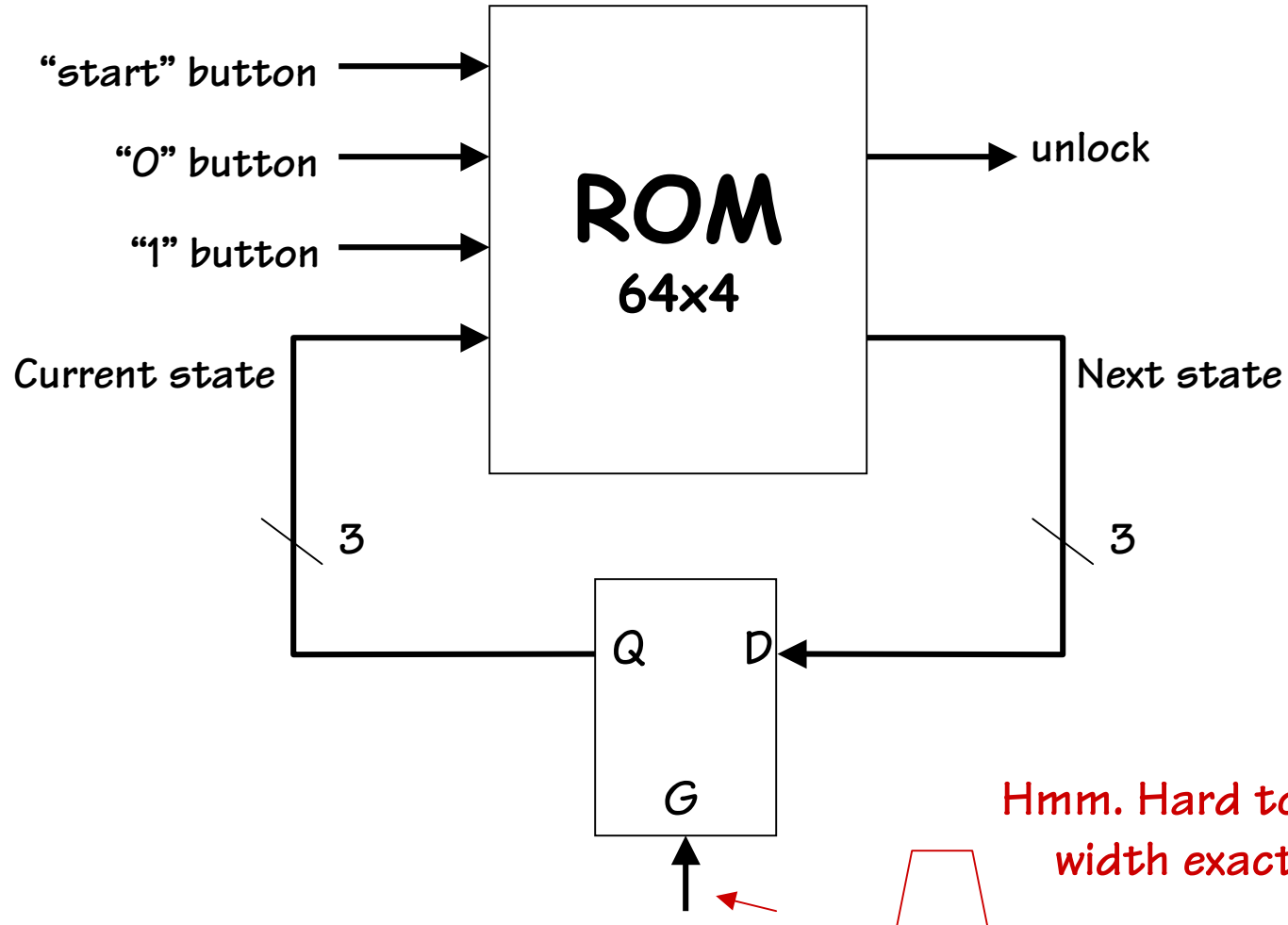we still haven't gotten a working implementation of an FSM




Two Gates are Better than One

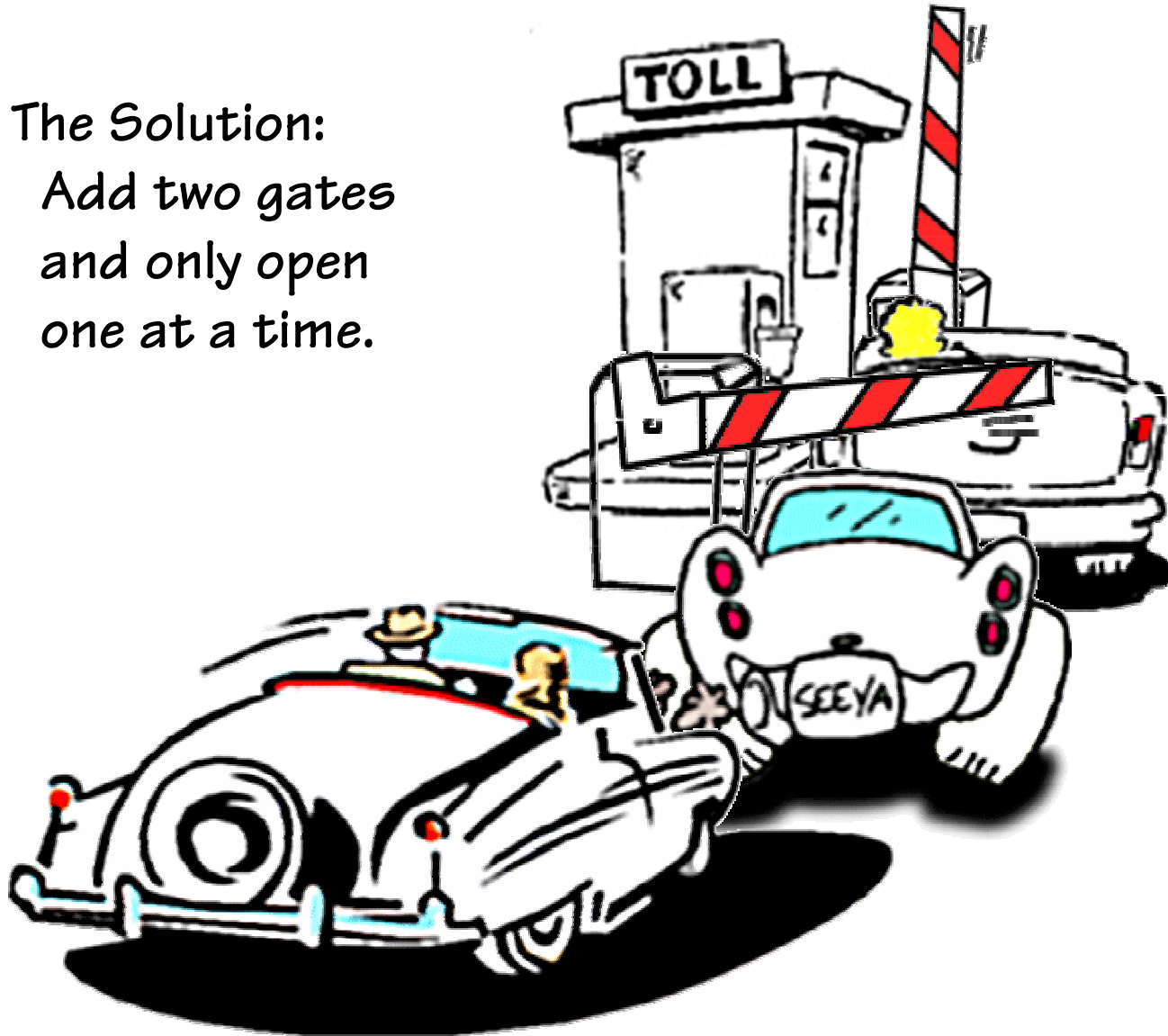The Solution:
Add two gates
and only open
one at a time.





Edge-triggered Flip Flop

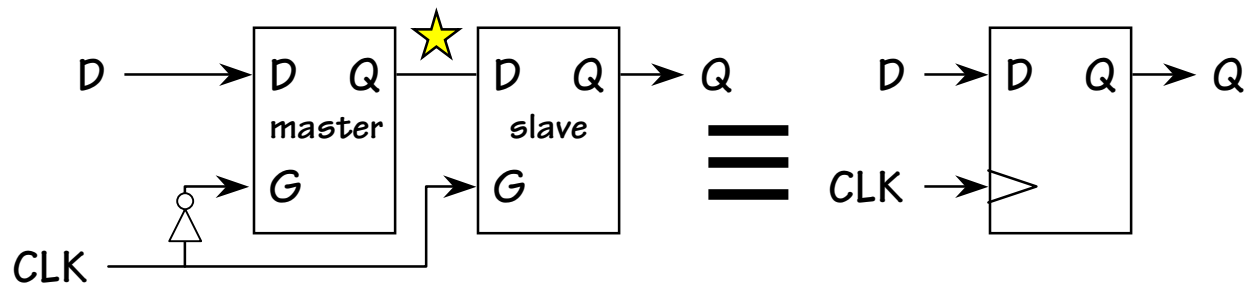


Observations:

- ♦ only one latch “transparent” at any time:
 - ♦ master closed when slave is open
 - ♦ slave closed when master is open→ no combinational path through flip flop
- ♦ Q only changes shortly after 0 → 1 transition of CLK, so flip flop appears to be “triggered” by rising edge of CLK

Flip Flop Waveforms

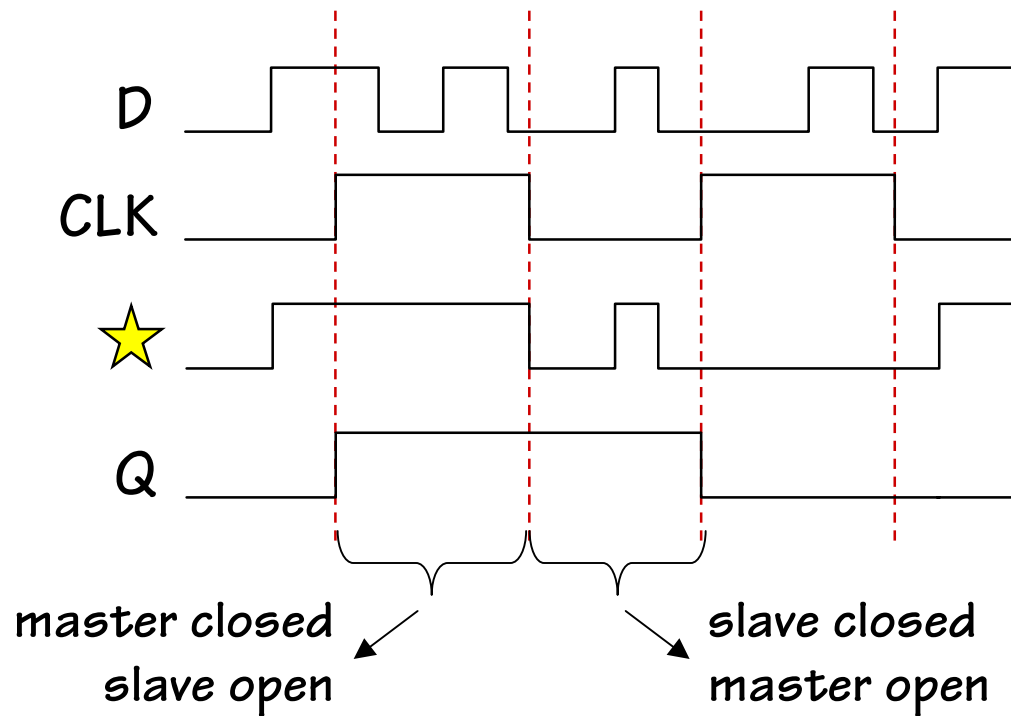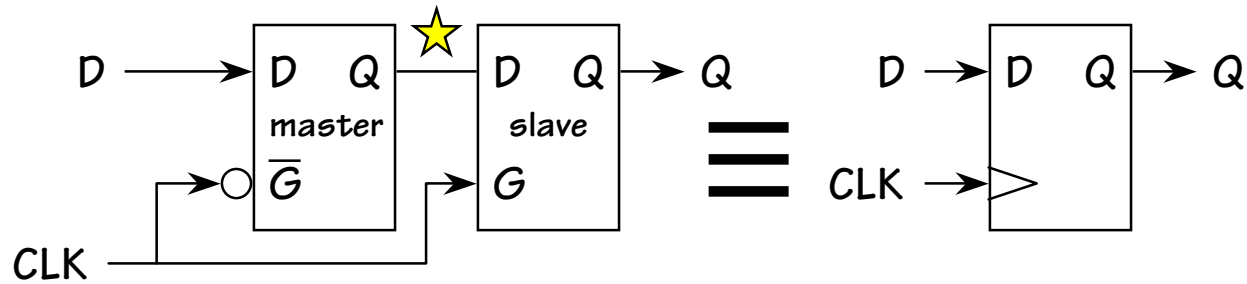

Um, about that hold time...


 


Consider HOLD TIME requirement for slave:

- Negative ($1 \rightarrow 0$) clock transition \rightarrow slave freezes data:
 - SHOULD be no output glitch, since master held constant data;
BUT
 - master output contaminated by change in G input!
- HOLD TIME of slave not met, UNLESS we assume sufficient contamination delay in the path to its D input!

Accumulated t_{CD} thru inverter, $G \rightarrow Q$ path of master must cover slave t_{HOLD} for this design to work!

Flip Flop Timing - I

  

t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{CD} : minimum contamination delay, CLK \rightarrow Q



t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

t_{HOLD} : hold time

guarantee master is closed and data is stable before allowing D to change

Flip Flop Timing - II

  

$$t_1 = t_{CD,reg1} + t_{CD,1} > t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,1} < t_{CLK} - t_{SETUP,reg2}$$


Questions for register-based designs:

- ♦ how much time for useful work (i.e. for combinational logic delay)?
- ♦ does it help to guarantee a minimum t_{CD} ? How 'bout designing registers so that

$$t_{CD,reg} > t_{HOLD} \quad ?$$

- ♦ what happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?

Example: Flip Flop Timing

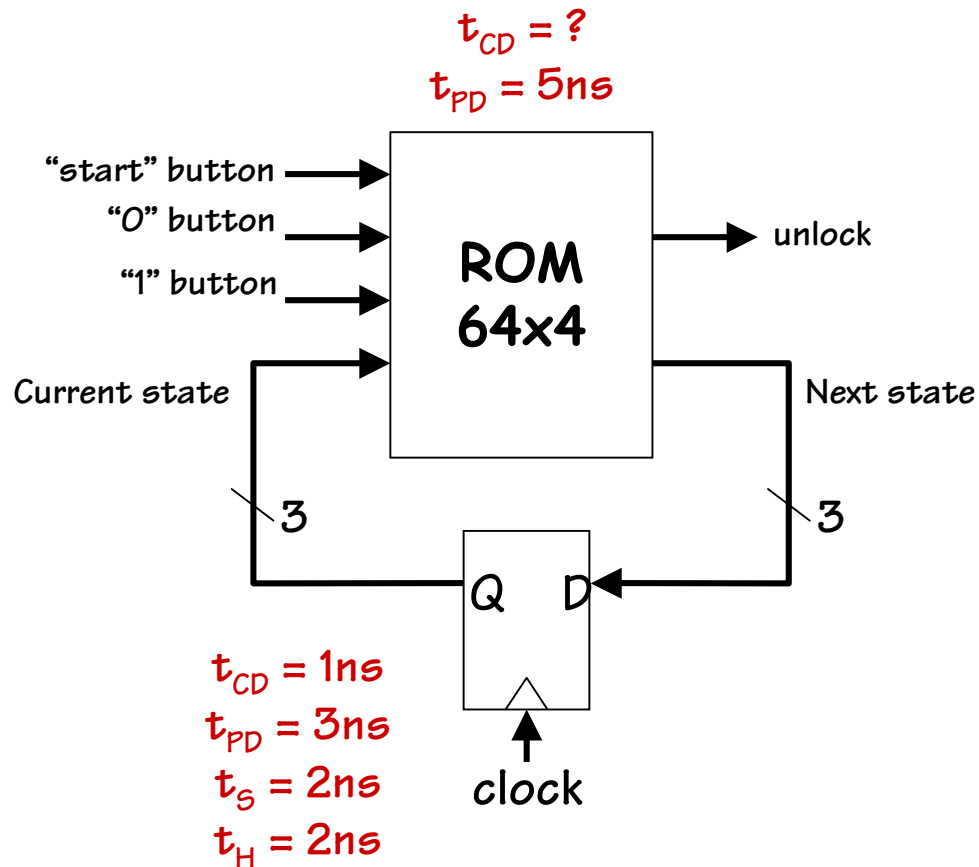


Questions:

1. t_{CD} for the ROM?
2. Min. clock period?
3. Constraints on inputs?

Single Synchronous Clock


A recipe for robust sequential circuits:

 

- No combinational cycles
- Only care about value of combinational circuits just before rising edge of clock
- Period greater than every combinational delay
- Change saved state after noise-inducing logic transitions have stopped!

Example FSM: Roboant®


8 legs?

 

SENSORS: antennae L and R, each 1 if in contact with something.


ACTUATORS: Forward Step F, ten-degree turns TL and TR (left, right).

 GOAL: Make our ant smart enough to get out of a maze like:




STRATEGY: "Right antenna to the wall"

Lost in space

 


 Action: Go forward until we hit something.




**“lost” is the
initial state**


Bonk!

 

 
Action: Turn left (CCW) until we don't touch anymore




A little to the right...

 

 
Action: Step and turn right a little, look for wall




Then a little to the left

 

 
Action: Step and turn left a little, till not touching (again)



Dealing with corners

 

 Action: Step and turn right until we hit perpendicular wall




Equivalent State Reduction

Observation: $S_i \equiv S_j$ if

 1. States have identical outputs; AND
2. Every input \rightarrow equivalent states.


Reduction Strategy:

Find pairs of equivalent states, **MERGE** them.



An Evolutionary Step

 Merge equivalent states Wall1 and Corner into a single new, combined state.



Behaves exactly as previous (5-state) FSM, but requires half the ROM in its implementation!

Roboant®

The screenshot displays the Roboant 2.0 software interface. On the left, a text editor window titled 'untitled' contains an FSM state table. The table is as follows:

now	L	R	S	next	L	R	F	M	E
lost	0	0	-	lost	0	0	1	0	0
lost	1	-	-	rotccw	0	0	1	0	0
lost	0	1	-	rotccw	0	0	1	0	0
rotccw	0	0	-	wall1	1	0	0	0	0
rotccw	1	-	-	rotccw	1	0	0	0	0
rotccw	0	1	-	rotccw	1	0	0	0	0
wall1	-	0	-	wall1	0	1	1	0	0
wall1	-	1	-	wall2	0	1	1	0	0
wall2	1	-	-	rotccw	1	0	1	0	0
wall2	0	1	-	wall2	1	0	1	0	0
wall2	0	0	-	wall1	1	0	1	0	0


Below the table, the status display shows: state: "lost", inputs: L=0 R=0 S=0; step 0

On the right, a maze simulation window shows a plan view of a maze with a pink robot at the top and a green ant at the bottom. The maze selection controls at the top of the window include radio buttons for m1 (selected), m2, m3, m4, and hampton. At the bottom of the window, simulation controls include a speed slider from Slow to Fast, and buttons for Reset, Step, Run, and Stop.

Annotations with red arrows point to the FSM state table, the maze selection controls, the plan view of the maze, the simulation controls, and the status display.

Featuring the new Mark-II ant: can add (M), erase (E), and sense (S) marks along its path.


Building the Transition Table

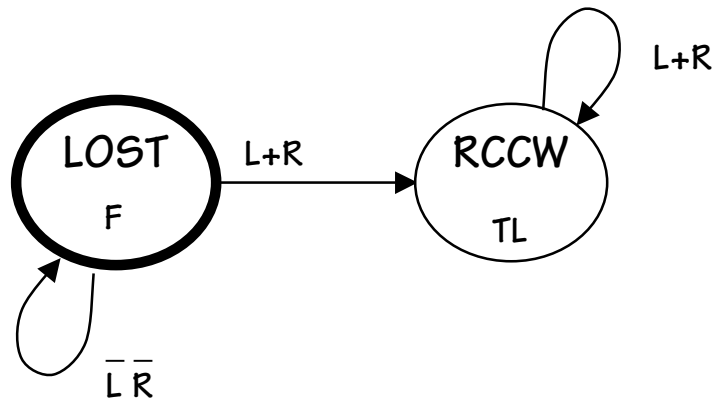


Implementation Details

LOST {
 RCCW {
 WALL1 {
 WALL2 {

Complete Transition table

 

 
$$S'_1 = S_1 \bar{S}_0 + \bar{L} S_1 + \bar{L} R S_0$$




$$S'_0 = R + \bar{L} \bar{S}_1 + L S_0$$

Ant Schematic

 

Finite State Machines: An important abstraction

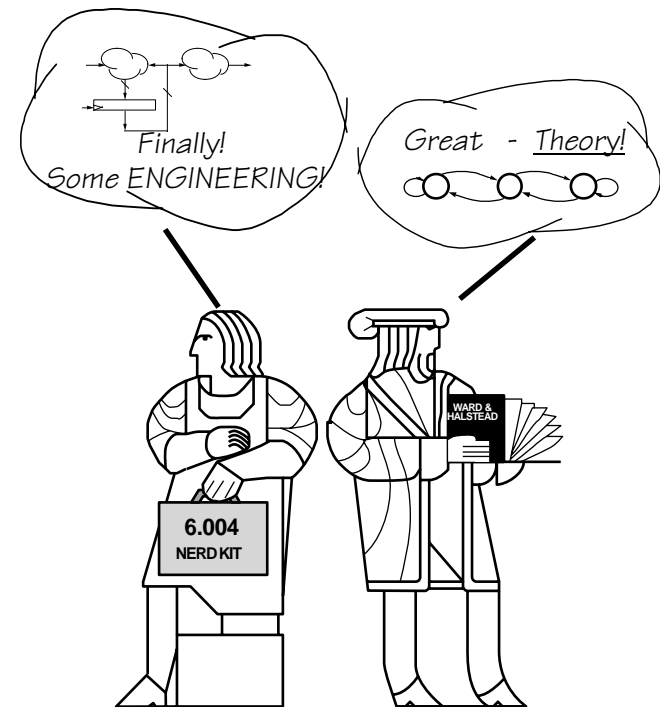- **FORMAL MODEL:**
Substantial theoretical results
 - **PRACTICAL IMPACT:**
Major engineering tool...
 - **METAPHYSICAL IMPACT:**
Are we all just complicated FSMs?
Perhaps with imperfect state registers
and “fuzzy” logic...
- ... You'll see FSMs for the rest of your life!





Summary

Synchronous 1-clock logic:

In order to build RELIABLE circuits we need only follow these simple rules.

  - 1) Clc period greater than:
 $FF(t_{pd}) + Logic(t_{pd}) + FF(t_{su})$
- 2) Satisfy hold time:
 $FF(t_{cd}) + Logic(t_{cd}) > FF(t_h)$
- 3) o combinational cycles



An essential element of the DYNAMIC DISCIPLINE is the specification of setup and hold times relative to a global clock edge.

